

CSCI 210: Computer Architecture

Lecture 19: State Elements

Stephen Checkoway

Oberlin College


Nov. 15, 2021

Slides from Cynthia Taylor

Announcements

- Problem Set 6 due Friday
- Lab 5 due Sunday
- Office Hours Tuesday 13:30 – 14:30

Last Class

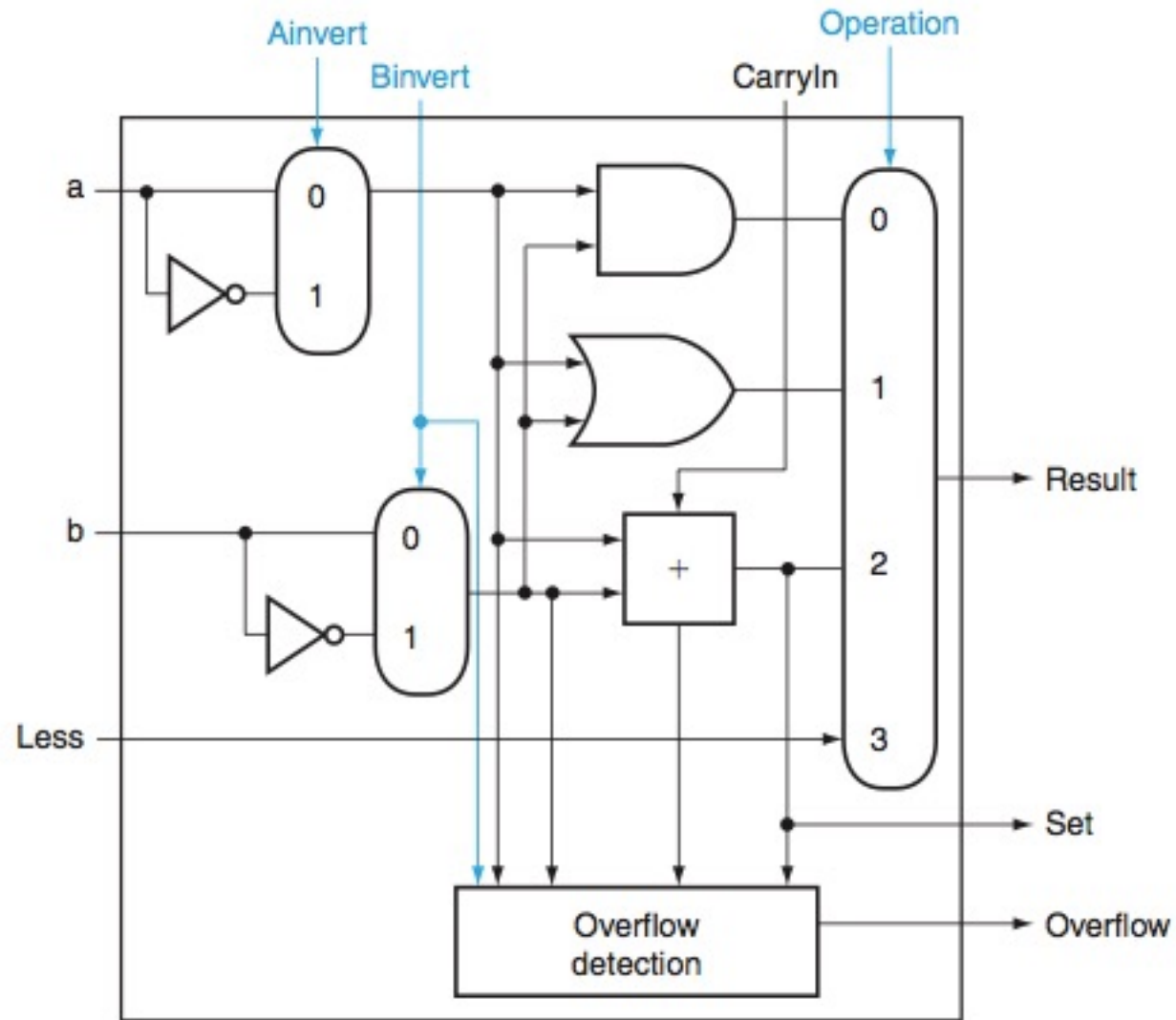

Adding Conditional Branching


- Want to be able to support beq, bne, etc
- Need to be able to check equality
- If $a = b$, then $a - b = 0$

Detect 0 in Multi-bit ALU

- Subtract $a - b$
- Take output from each 1-bit ALU

We know Result0-31 are 0 if we perform a _____ operation on Result0 through Result31, and it outputs _____

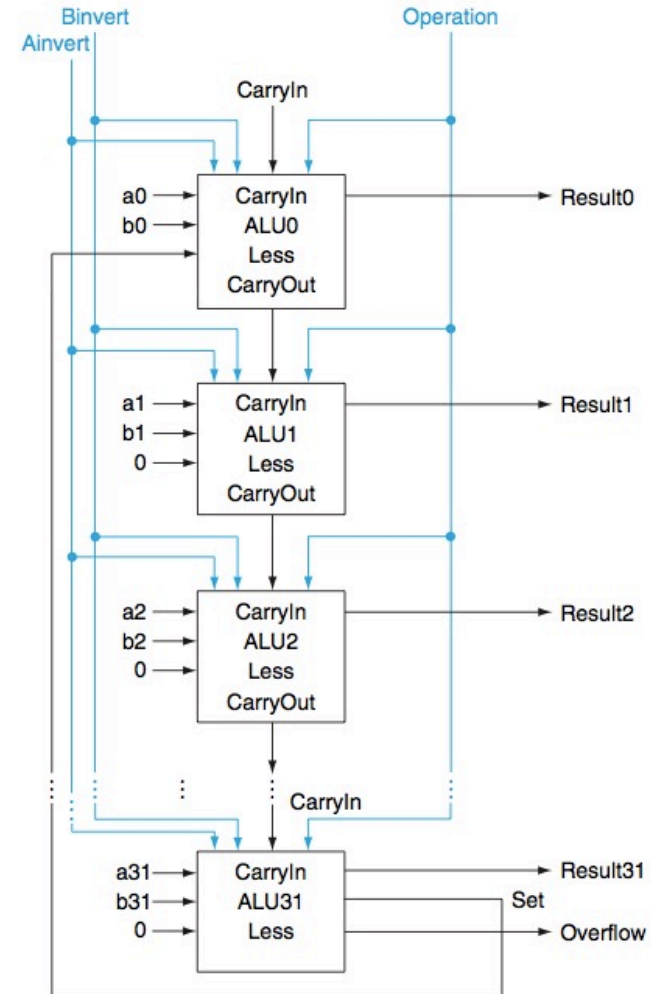
- A. AND, 0
- B. OR, 0
- C. NAND, 1
- D. XOR, 0
- E. None of the above




Detect 0 in Multi-bit ALU

- Subtract $a - b$
- Take output from each 1-bit ALU
- OR outputs together
 - If any output is 1, result will be 1, else 0
- Negate the result


Multi-bit ALU with zero check

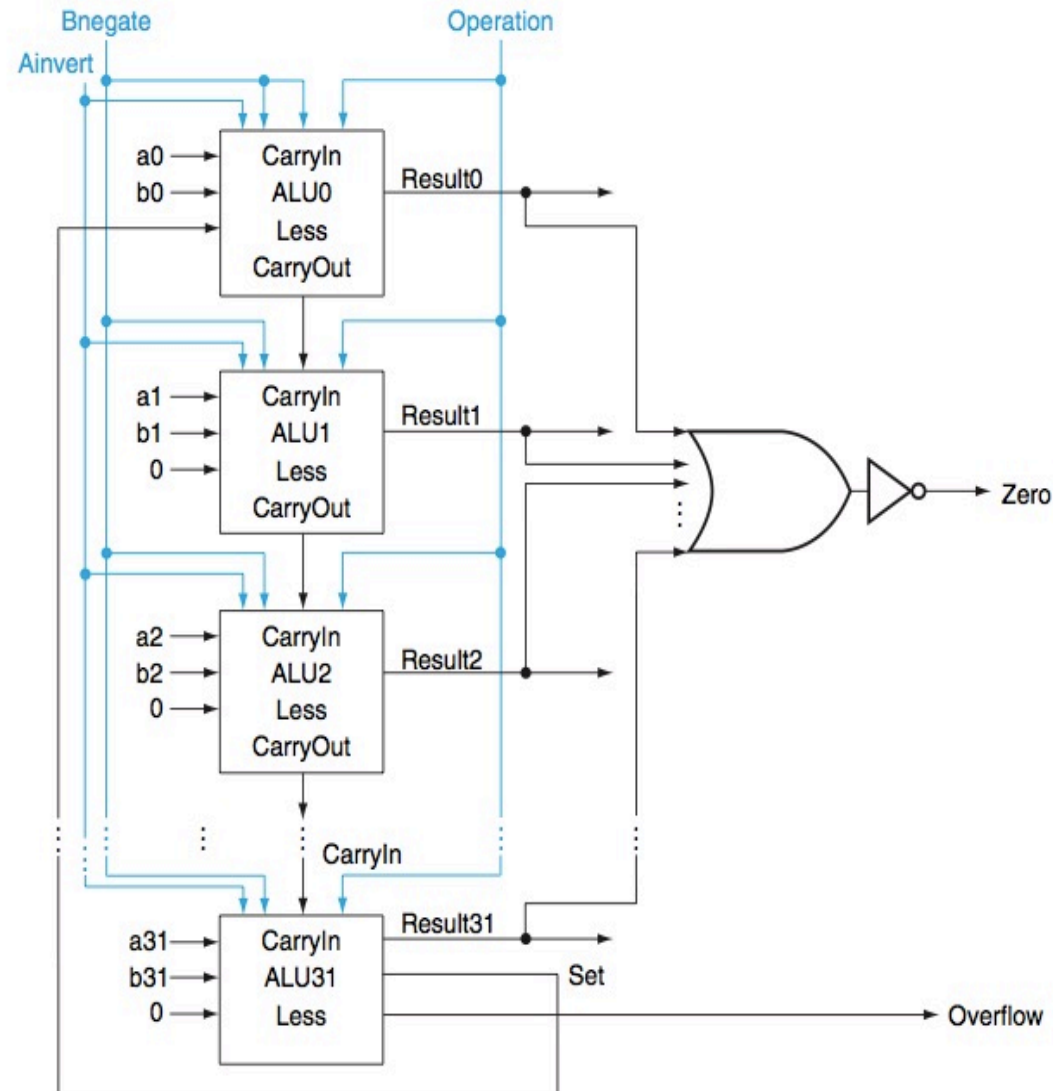


Symbol for Multi-bit ALU

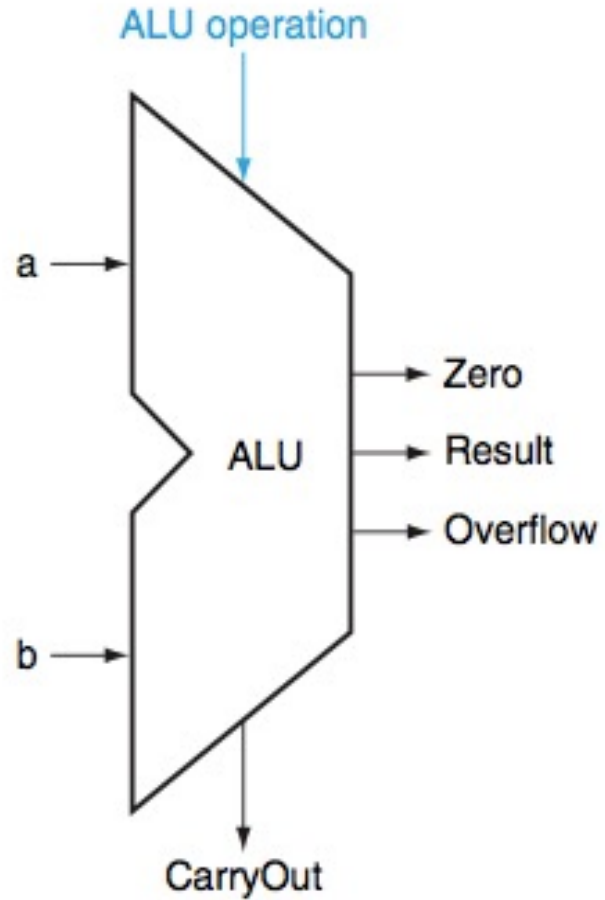

Logic Gates and Timing

 

 Which of the following most closely maps to Y (the output of the inverter)?





Inverter

X Y


0 1

1 0

  

E None of the above.

Select the correct output for Y

 

AND


JK Y

00 0


01 0

10 0

11 1

 


E None of the above


 


AND gate waveforms

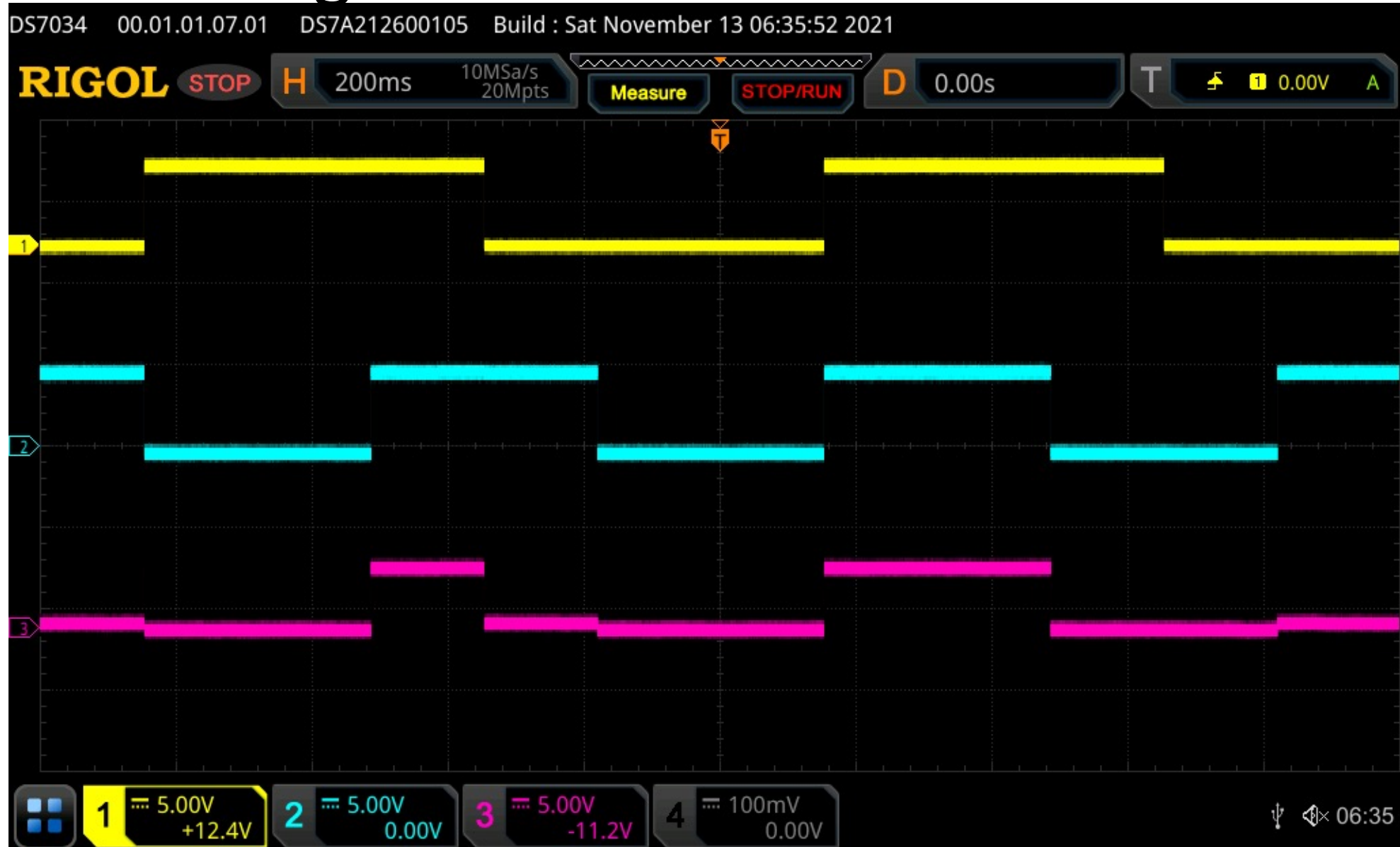- Inputs
 - Yellow
 - Blue
- Output
 - Pink




Two Types of Logic Components

  

State Elements


- Output depends on input, AND a value saved inside the element
- Have *memory*

Set-Reset (S-R) Latch

 


- Output depends on S, R, AND previous value of Q
- Stores 1 bit of state

S-R Latch: $S = 1, R = 0$

 


	Q
A	0
B	1
C	Q from before
D	\bar{Q} from before
E	None of the above

S-R Latch: $S = 0, R = 1$

 


	Q
A	0
B	1
C	Q from before
D	\bar{Q} from before
E	None of the above

S-R Latch: $S = 0, R = 0$

 


	Q
A	0
B	1
C	Q from before
D	\bar{Q} from before
E	None of the above

S-R Latch: $S = 1, R = 1$

 

	Q
A	0
B	1
C	Q from before
D	\bar{Q} from before
E	None of the above

S-R Latch

 

- Set: $Q_i = 1$
- Reset: $Q_i = 0$
- Otherwise, $Q_i = Q_{i-1}$

Terminology

- The S-R latch is a **bistable multivibrator**
 - Bistable: two stable states—set $Q = 1, \bar{Q} = 0$ and reset $Q = 0, \bar{Q} = 1$
 - Monostable: one stable state, one unstable state; the circuit returns to the stable state after a short time in the unstable state
 - Astable: two unstable states and the circuit switches between them
 - Multivibrator: a digital circuit that uses feedback
 - The name comes from the first such circuit that produced a square wave which had many harmonics, hence *multivibrateur*

Clock



- Oscillates between 1 and 0 at a set rate
- Used with elements that have memory

Clocked SR Latch


 
 


Figure 3-23. A clocked SR latch.

- Only changes state when the clock is asserted

Given S, R and Clock, Q will be:

 

D. None of the above

Reading

- Next lecture: Clocks, Latches and Flip flops
– 3.7
- Problem Set 6 due Friday
- Lab 5 due Sunday