

CSCI 210: Computer Architecture  
Lecture 20: Clocks, Latches and Flip-Flops

Stephen Checkoway

Oberlin College

Apr. 13, 2022


Slides from Cynthia Taylor

# Announcements


- Problem Set 6 due Friday
- Lab 5 due a week from Sunday
- Office Hours Friday 13:30–14:30
 
# S-R Latch


- Set:  $Q_t = 1$        $\bar{Q}_t = 0$
- Reset:  $Q_t = 0$        $\bar{Q}_t = 1$
- Otherwise:  $Q_t = Q_{t-1}$        $\bar{Q}_t = \bar{Q}_{t-1}$



 We can also build S-R latches out of NAND gates




 The logic is inverted: set and reset are 0-triggered






 
The logic is inverted: set and reset are 0-triggered



 $S = 0, R = 0$  is the invalid combination



 When S and R are released (brought to 1) simultaneously, it's astable





# Clock



- Oscillates between 1 and 0 with a fixed period
  - 0 to 1 transition is a **rising edge**
  - 1 to 0 transition is a **falling edge**
  - Time between two rising (or falling) edges is one **period** or **cycle**
- Used to control when values change

# Clocked S-R Latch

 


Figure 3-23. A clocked SR latch.

- Only changes state when the clock is asserted

Given S, R and Clock, Q will be:



 


Figure 3-23. A clocked SR latch.

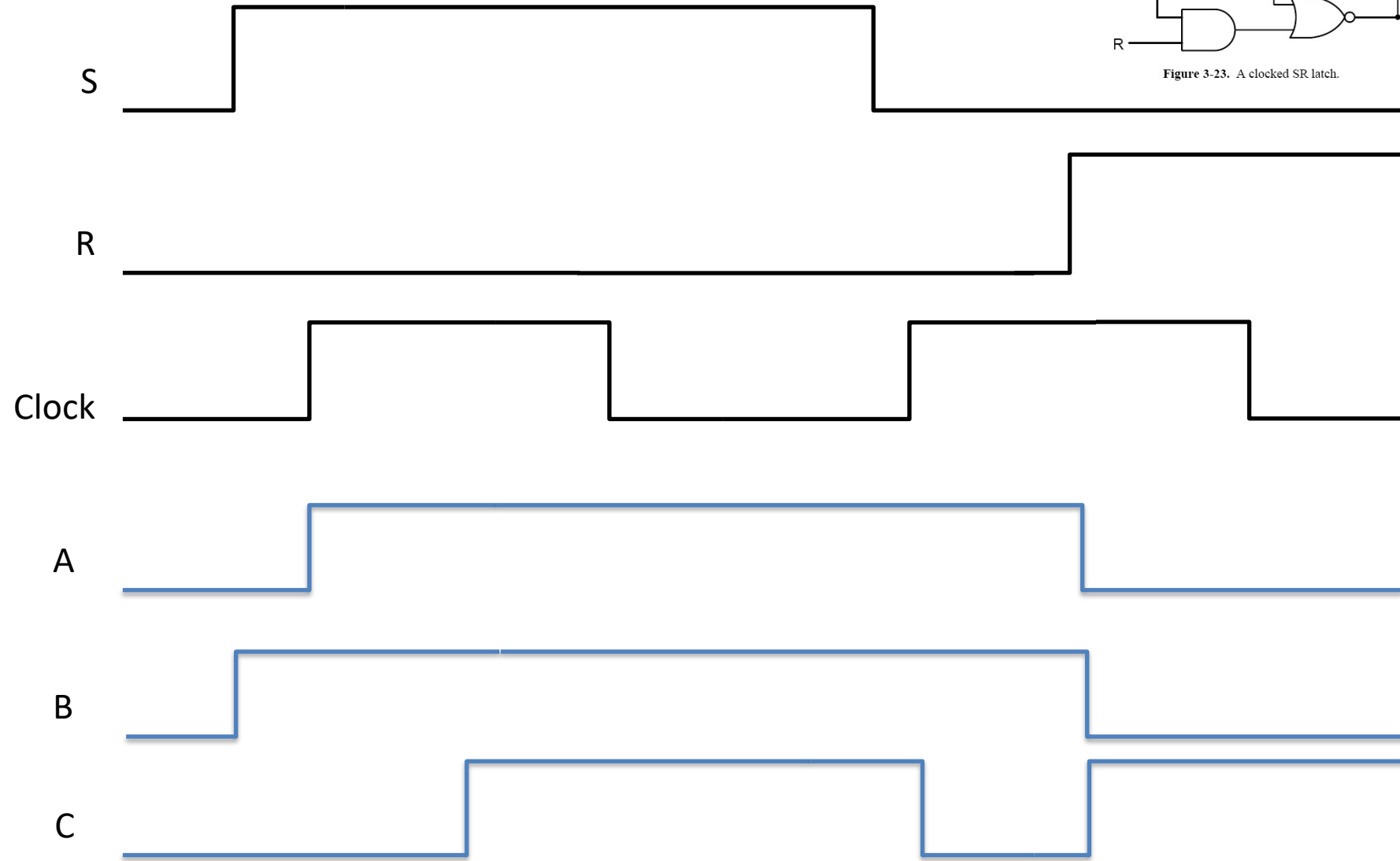


D. None of the above

# Clocked D-Latch

 

- S-R latch, but now there is a single input, D, ANDed with the clock (labeled C rather than the more normal clk)
- Now impossible to have both inputs set to 1
 
# Which Column Completes the Truth Table?




C	D	Q
1	1	
1	0	

A	B	C	D
1	1	0	1
1	0	1	$Q_{\text{prev}}$

E. None of the above


 
# Which Column Completes the Truth Table?




C	D	Q
0	1	
0	0	

A	B	C	D
0	1	1	$Q_{\text{prev}}$
0	0	$Q_{\text{prev}}$	$Q_{\text{prev}}$



E. None of the above

# Clocked D-Latch

 


- Latch is “open” when clock is asserted (asserted = logical 1)
- $Q$  = value of  $D$  when the latch is open
- $Q$  = most recently set value when the latch is closed

  Clocked D-Latch; note output takes a little time to change after the clock goes high




# D Flip-Flop

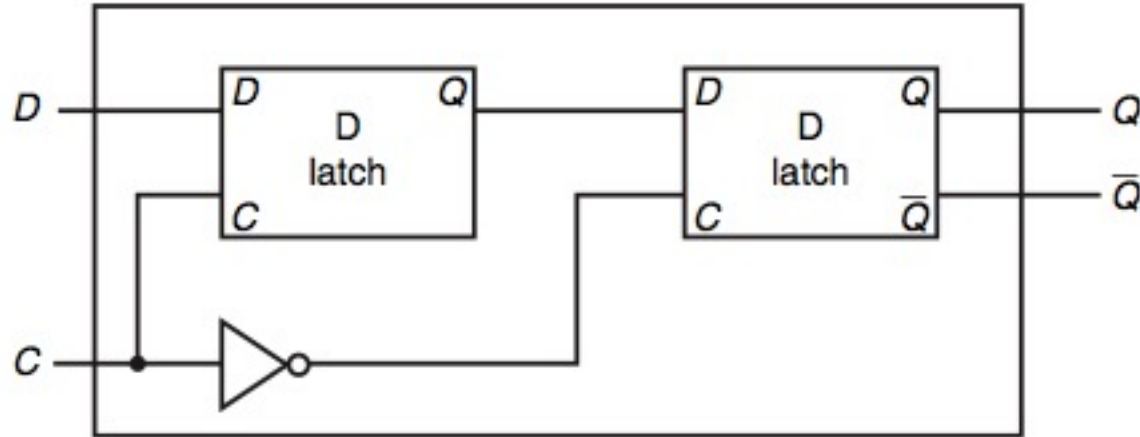

- Two D-Latches, with the clock negated to the second latch


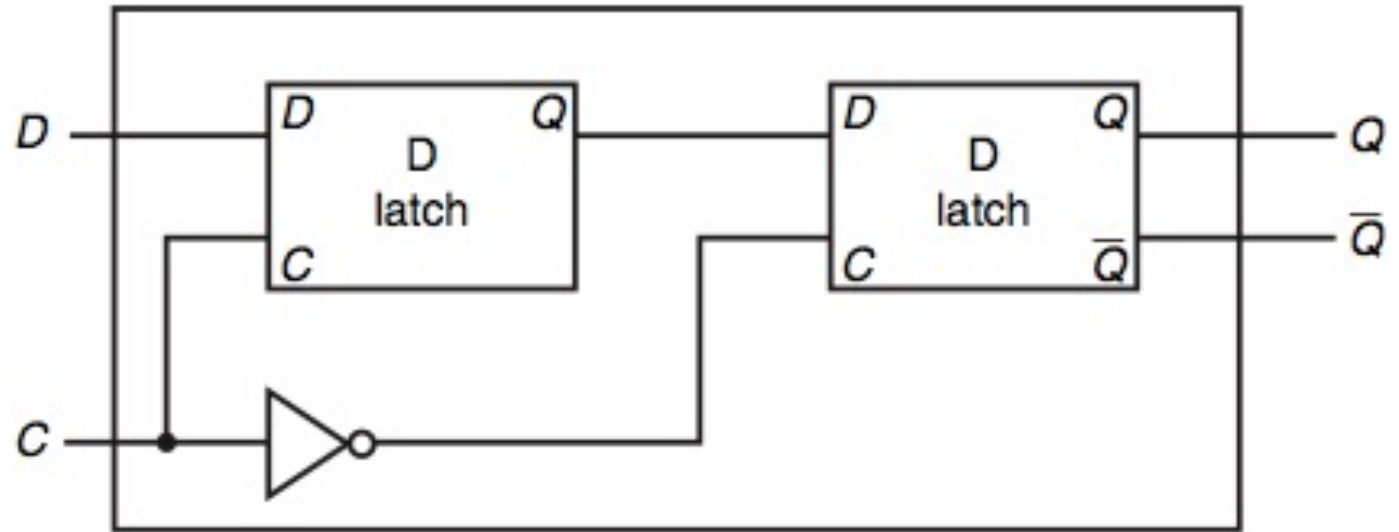
# The value of (the right-most) Q can change




- A. Any time the clock is 1.
- B. Any time the clock is 0.
- C. When the clock changes from 1 to 0.
- D. When the clock changes from 0 to 1.
- E. None of the above



# D-flip-flop: Falling Edge Trigger

  


# Edge-triggering

 

- All changes to state happen at one point in the clock cycle (either rising edge, or falling edge).
- (This is an unusual clock with a 75% duty cycle—it's on 75% of the time—most clocks have a 50% duty cycle)


# Memory

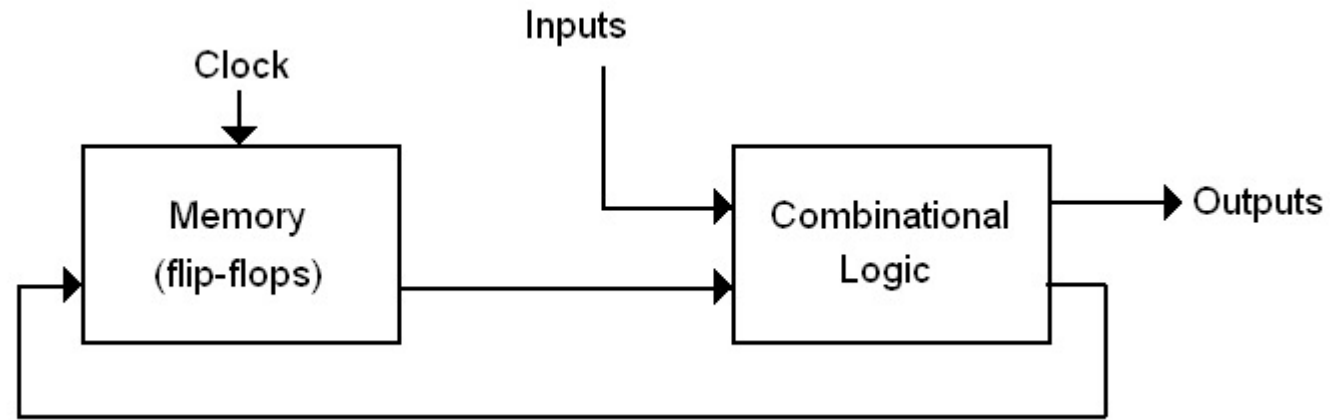


- Can save the results of combinational logic (think the ALU)
- Registers are (multi-bit) flip-flops!
 
# Registers

- Each 32-bit register will consist of 32 1-bit D flip-flops




# Register File

 


- Set of registers that can be written/read by supplying a register number
- MIPS has a register file with thirty-two 32-bit registers



# Read Function

 

# Write Function

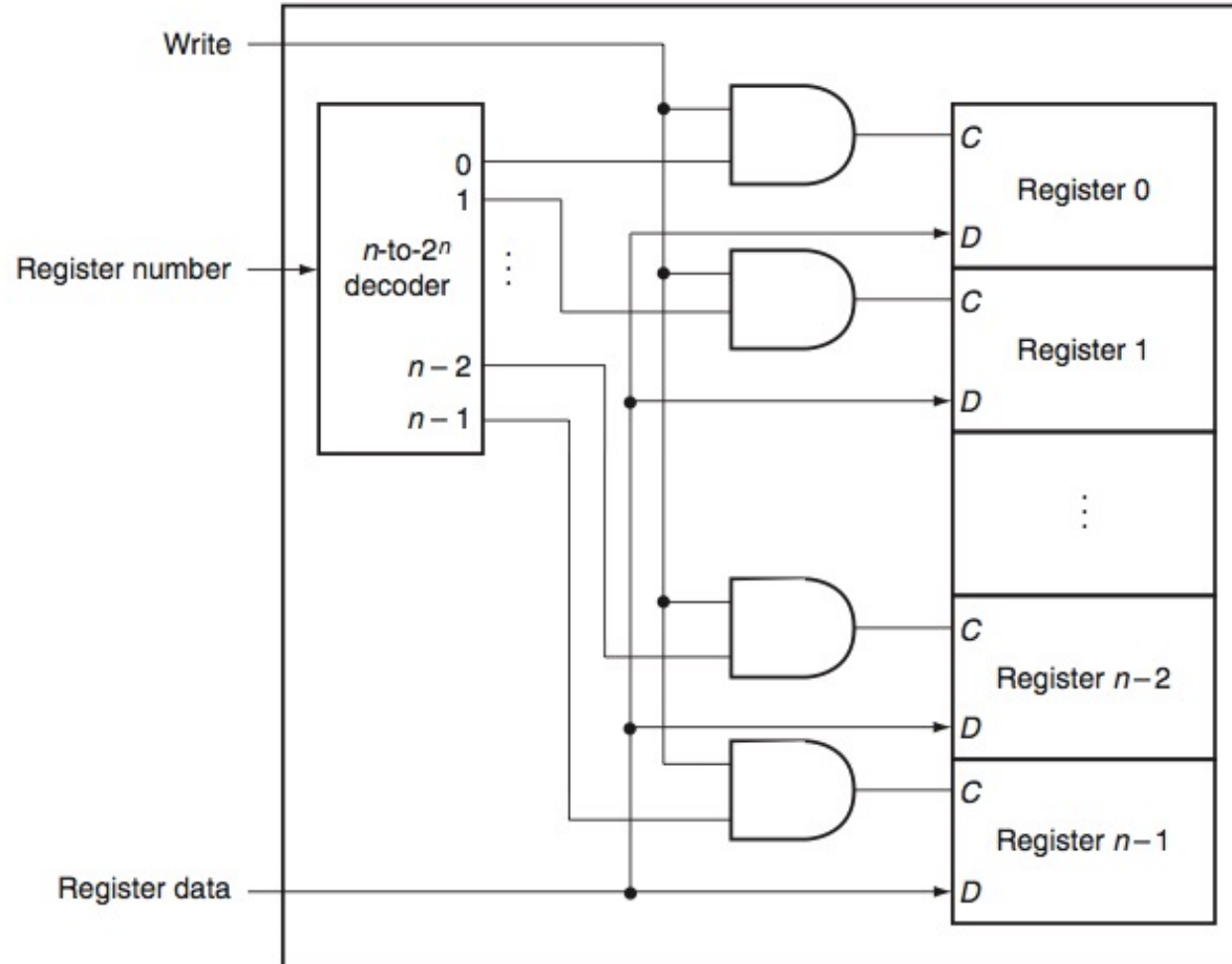

\*The image is not quite correct. It should be a  $\lg n$  to  $n$  decoder

In MIPS, we have 32 registers so we need a 5-to-32 decoder, not a 32-to-4294967296 decoder!

What will happen if we read and write to a register  
in the same clock cycle?

- A. The read will get the original value
- B. The read will get the just written value
- C. It is ambiguous
- D. None of the above

# Reading

- Next lecture: Floating Point
  - 4.4
- Problem Set 6 due Friday