

CSCI 210: Computer Architecture

Lecture 15: Boolean Algebra

Stephen Checkoway

Slides from Cynthia Taylor

CS History: Augustus de Morgan



- British, born in 1871
- Published De Morgan's Laws in 1947
- Introduced the term induction
- Didn't receive an MA from Cambridge because it required passing a theological test and he was an atheist
- Ada Lovelace was his student
- Dedicated to making scientific knowledge available to the public – wrote numerous articles about many topics

Boolean Algebra

- Branch of algebra in which all variables are 1 or 0 (equivalently true or false)
- Introduced by George Boole in 1847
- Multiple notations
 - $x \wedge y$ $x \vee y$
 - xy $x + y$

Boolean laws

- Commutativity $x + y = y + x$ $xy = yx$
- Associativity $x + (y + z) = (x + y) + z$ $x(yz) = (xy)z$
- Distributivity $x + yz = (x + y)(x + z)$ $x(y + z) = xy + yz$
- Idempotence $x + x = x$ $xx = x$

Which Identity Laws Are True?

A. $x + 0 = x$, $x0 = x$

B. $x + 0 = x$, $x1 = x$

C. $x + 1 = x$, $x0 = x$

D. $x + 1 = x$, $x1 = x$

E. None of the above

Which Complementation Laws Are True?

A. $\bar{x} + x = 0, \quad \bar{x}x = 0$

B. $\bar{x} + x = 0, \quad \bar{x}x = 1$

C. $\bar{x} + x = 1, \quad \bar{x}x = 0$

D. $\bar{x} + x = 1, \quad \bar{x}x = 1$

E. None of the above

Which Annihilator Laws Are True?

A. $x + 0 = 0, \quad x0 = 0$

B. $x + 1 = 1, \quad x0 = 0$

C. $x + 0 = 0, \quad x1 = 1$

D. $x + 1 = 1, \quad x1 = 1$

E. None of the above

Simplifying Expressions

$$F = XYZ + XY\bar{Z} + \bar{X}Z$$

- A. $F = XY + \bar{X}Z$
B. $F = X(YZ + Y\bar{Z} + Z)$
C. $F = XY(Z + \bar{Z}) + \bar{X}Z$
D. This cannot be simplified further

- Identity law: $A + 0 = A$ and $A \cdot 1 = A$
- Zero and One laws: $A + 1 = 1$ and $A \cdot 0 = 0$
- Inverse laws: $A + \bar{A} = 1$ and $A \cdot \bar{A} = 0$
- Commutative laws: $A + B = B + A$ and $A \cdot B = B \cdot A$
- Associative laws: $A + (B + C) = (A + B) + C$ and $A \cdot (B \cdot C) = (A \cdot B) \cdot C$
- Distributive laws: $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ and $A + (B \cdot C) = (A + B) \cdot (A + C)$

Simplifying Expressions

$$F = XYZ + XY\bar{Z} + \bar{X}Z$$

- Identity law: $A + 0 = A$ and $A \cdot 1 = A$
- Zero and One laws: $A + 1 = 1$ and $A \cdot 0 = 0$
- Inverse laws: $A + \bar{A} = 1$ and $A \cdot \bar{A} = 0$
- Commutative laws: $A + B = B + A$ and $A \cdot B = B \cdot A$
- Associative laws: $A + (B + C) = (A + B) + C$ and $A \cdot (B \cdot C) = (A \cdot B) \cdot C$
- Distributive laws: $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ and $A + (B \cdot C) = (A + B) \cdot (A + C)$

DeMorgan's Law

- DeMorgan's Law
 - Use to obtain the complement of an expression

$$\overline{x + y} = \bar{x} \cdot \bar{y}$$

$$\overline{xy} = \bar{x} + \bar{y}$$

What is $\overline{AB + AC}$?

A. $\bar{A}B + \bar{A}C$

B. $(\bar{A}B)(\bar{A}C)$

C. $(A + B)(A + C)$

D. $(\bar{A} + B)(\bar{A} + C)$

E. None of the above

$$\overline{x + y} = \bar{x} \cdot \bar{y}$$

$$\overline{xy} = \bar{x} + \bar{y}$$

Questions on Boolean Algebra?

Sum of Products form of Boolean function f

- Developed from the truth table for $f(x_1, \dots, x_n)$
- Find all the rows of the truth table in which $f = 1$
- By definition, $f(x_1, \dots, x_n) = 1$ if and only if the input x_1, \dots, x_n match one of these rows
- We can write f as an OR (sum) of expressions checking if the input matches one of the rows:
 - $f = (\text{input matches row 1}) \text{ OR } (\text{input matches row 4}) \text{ OR } \dots$

Sum of Products

- Developed from the truth table
 - Each product term contains each input exactly once, complemented or not.
 - Need to OR together set of AND terms to satisfy table
 - One product for each 1 in F column

X	Y	F
0	0	0
0	1	1
1	0	1
1	1	0

What is the Sum of Products of F?

A. $\bar{A} + B\bar{C}$

B. $A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}C$

C. $\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C}$

D. $ABC + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}C + \bar{A}BC$

E. None of the above

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Product of Sums

- Express the same function as the AND of ORs
- Write out the sum of products for F and then take the complement using DeMorgan's law

X	Y	F
0	0	0
0	1	1
1	0	1
1	1	0

Product of Sums

- Simplified: Select the rows where F is 0 and take the complements of the inputs to form the ORs


X	Y	F
0	0	0
0	1	1
1	0	1
1	1	0

What is the Product of Sums of F?

A. $F = (A + B + C)(A + B + C)(A + B + C)$	A	B	C	F
	0	0	0	1
	0	0	1	1
B. $F = (\bar{A} + B + C)(\bar{A} + B + C)(\bar{A} + B + C)$	0	1	0	1
	0	1	1	1
C. $F = (A + \bar{B} + \bar{C})(A + \bar{B} + C)(A + B + C)$	1	0	0	0
	1	0	1	0
	1	1	0	1
D. $F = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(A + \bar{B} + \bar{C})(A + B + \bar{C})$	1	1	1	0

Programmable Logic Array

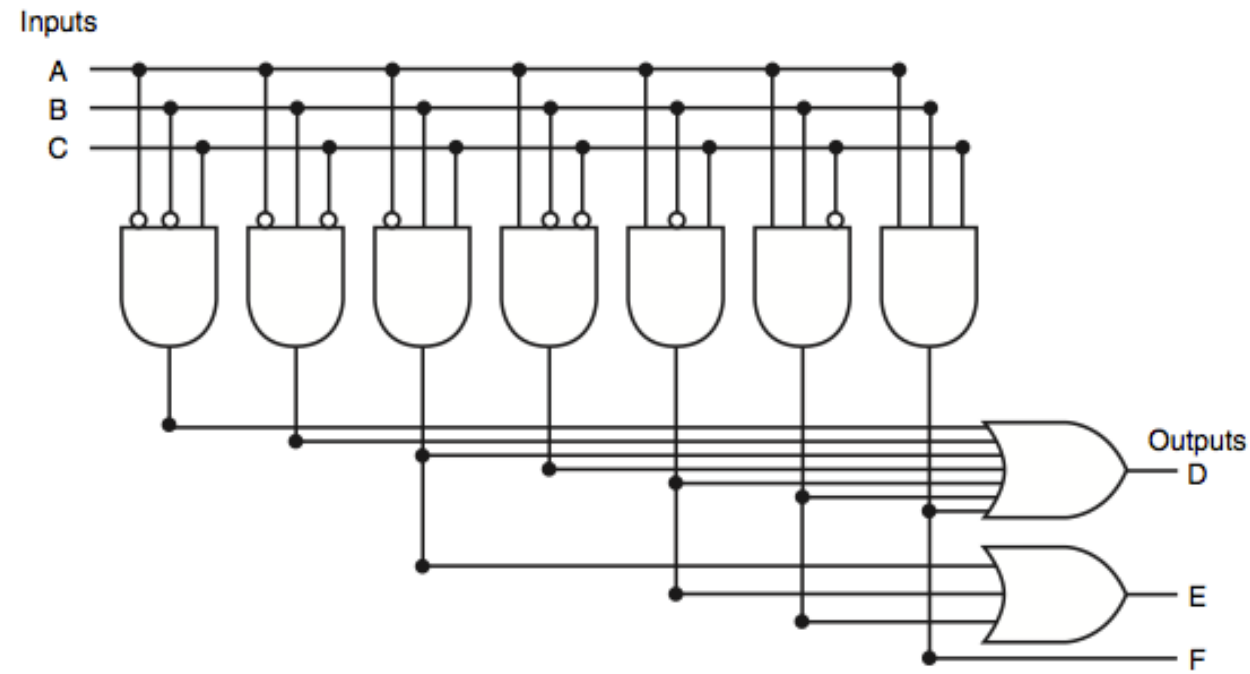- Simple way to create a logical circuit from a truth table, using sum of products
- Set of inputs and inverted inputs
- Array of AND gates
 - Form set of product terms
- Array of OR gates
 - Logical sum of product terms



Uses

- Either programmed during manufacture, or can be reprogrammed
- Used in CPUs, microprocessors

Creating a PLA

- Prepare the truth table
- Write the Boolean expression in sum of products form.
- Decide the input connection of the AND matrix for generating the required product term.
- Then decide the input connections of OR matrix to generate the sum terms.
- Program the PLA.

Size

- Only truth table entries that have a True (1) output are represented
- Each different product term will have only one entry in the PLA, even if the product term is used in multiple outputs

Multiple outputs


Inputs			Outputs		
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>E</i>	<i>F</i>
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

Output functions: $D(A, B, C)$, $E(A, B, C)$, $F(A, B, C)$

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

Sum of Products for output D	
A	$\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$
B	$\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$
C	$(A+B+\bar{C})(A+B+C)(A+B+\bar{C})(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$
D	$\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$

Inputs

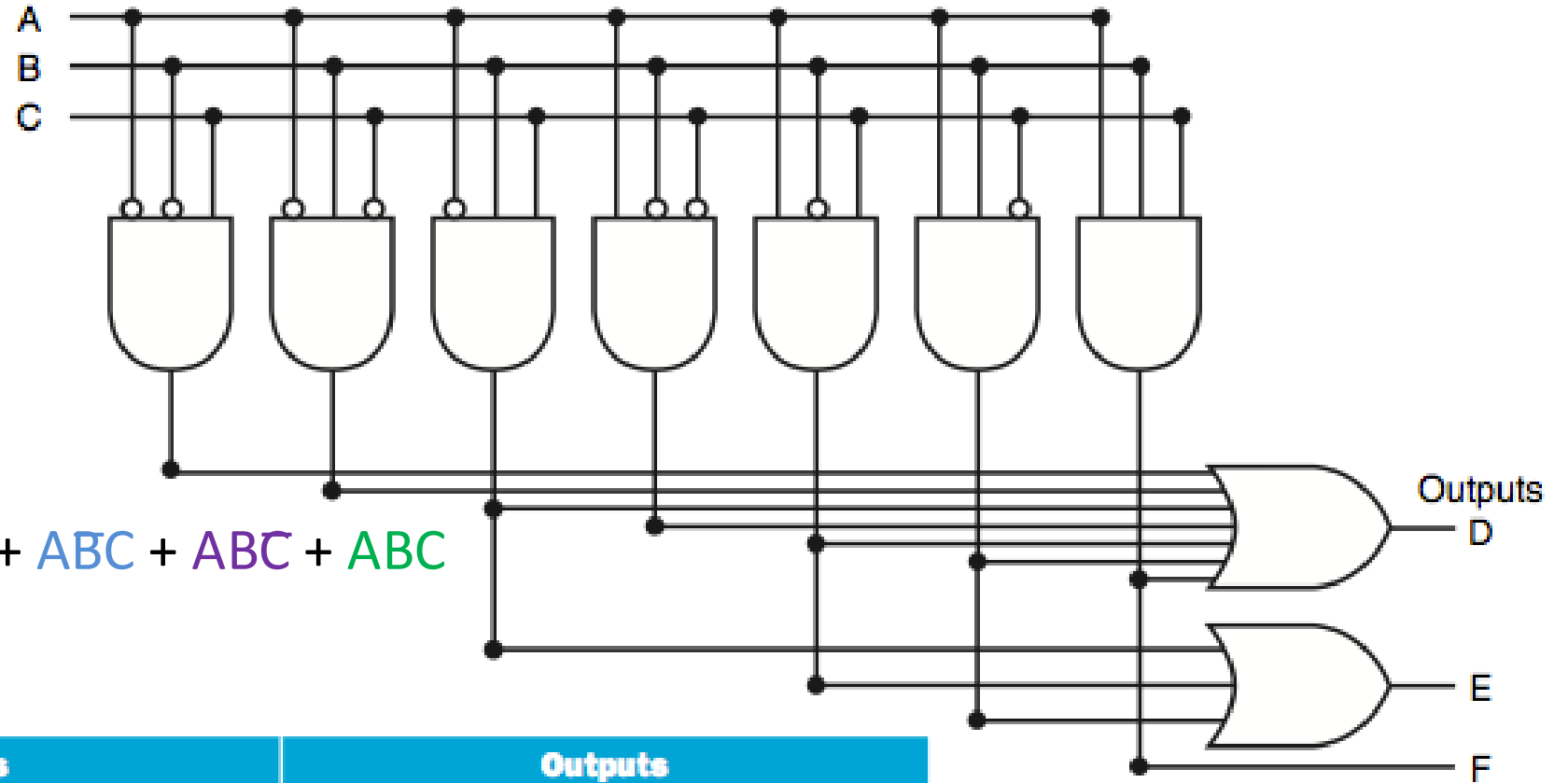

$$D = \bar{A}BC + A\bar{B}C + \bar{A}BC + ABC + A\bar{B}C + \bar{A}BC + ABC$$

$$E = \bar{A}BC + A\bar{B}C + \bar{A}BC$$

$$F = ABC$$

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

Field Programmable PLAs

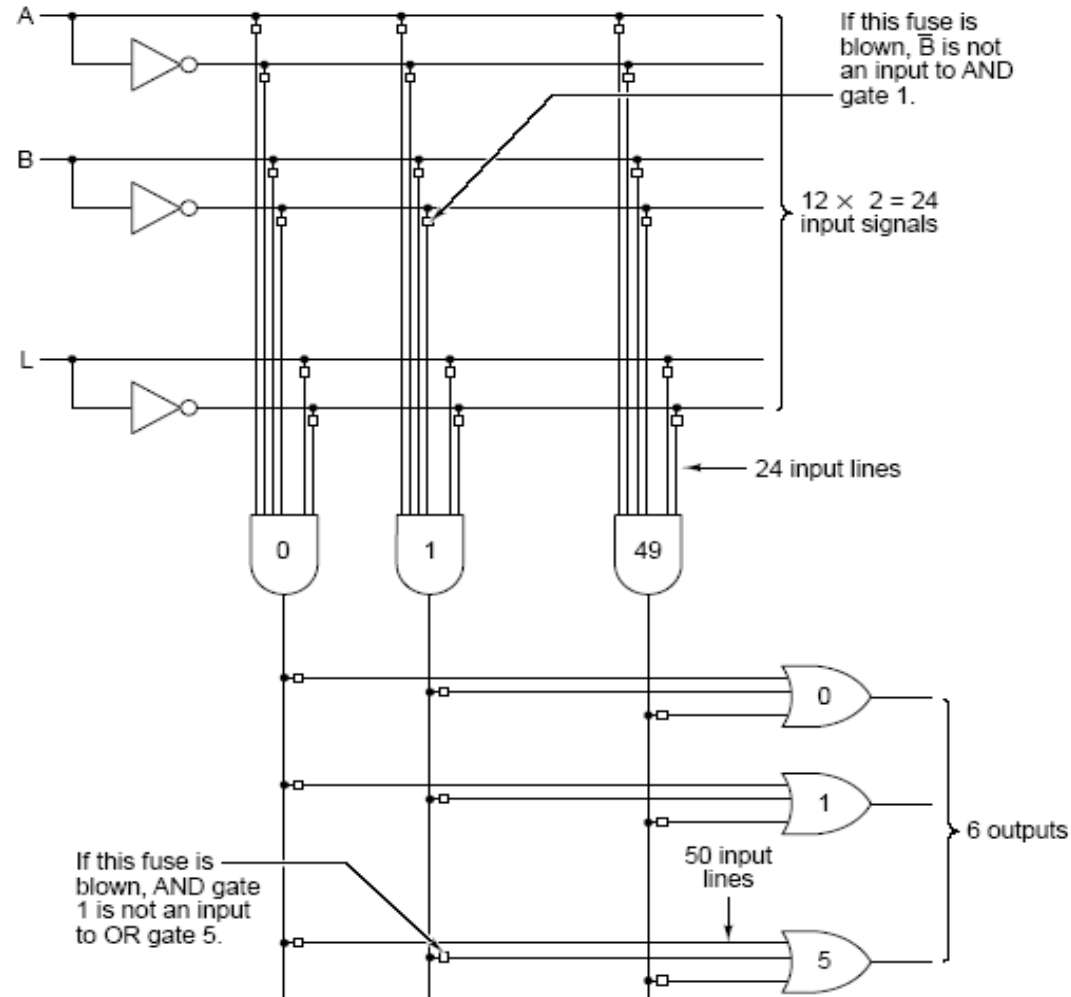


Figure 3-15. A 12-input, 6-output programmable logic array.

Reading

- Next lecture: Combinational Logic
 - Section 3.3 (Skip Don't Cares section)