

CSCI 210: Computer Architecture

Lecture 25: Data Path 2



Stephen Checkoway

Slides from Cynthia Taylor

Announcements

- Problem Set 8 Due TONIGHT 10pm
 - Problem Sets 5 and 6 graded, resubmits up
- Lab 7 due Monday 10 pm
- Computational Skills Hours, King 225
 - Wednesday, Sunday 7 – 9 pm
- Cynthia's Student Hours King 139 B
 - Monday 4:30 – 5:30 pm
 - Thursday 10 am – noon

CS History: Intel 4004

  


- First commercially available microprocessor (single chip with both data processing logic and control)
- Released in 1971
- Had 12-bit addresses, 8-bit instructions, and 4-bit data words
- 16 4-bit registers
- Designed for Binary-Coded Decimal, in which every decimal digit is stored as a 4-bit value
 - Still present in x86

The Processor: Datapath & Control

- We're ready to look at an implementation of MIPS simplified to contain only:
 - memory-reference instructions: `lw, sw`
 - arithmetic-logical instructions: `add, sub, and, or, slt`
 - control flow instructions: `beq`

lw \$t1, 4(\$t0)

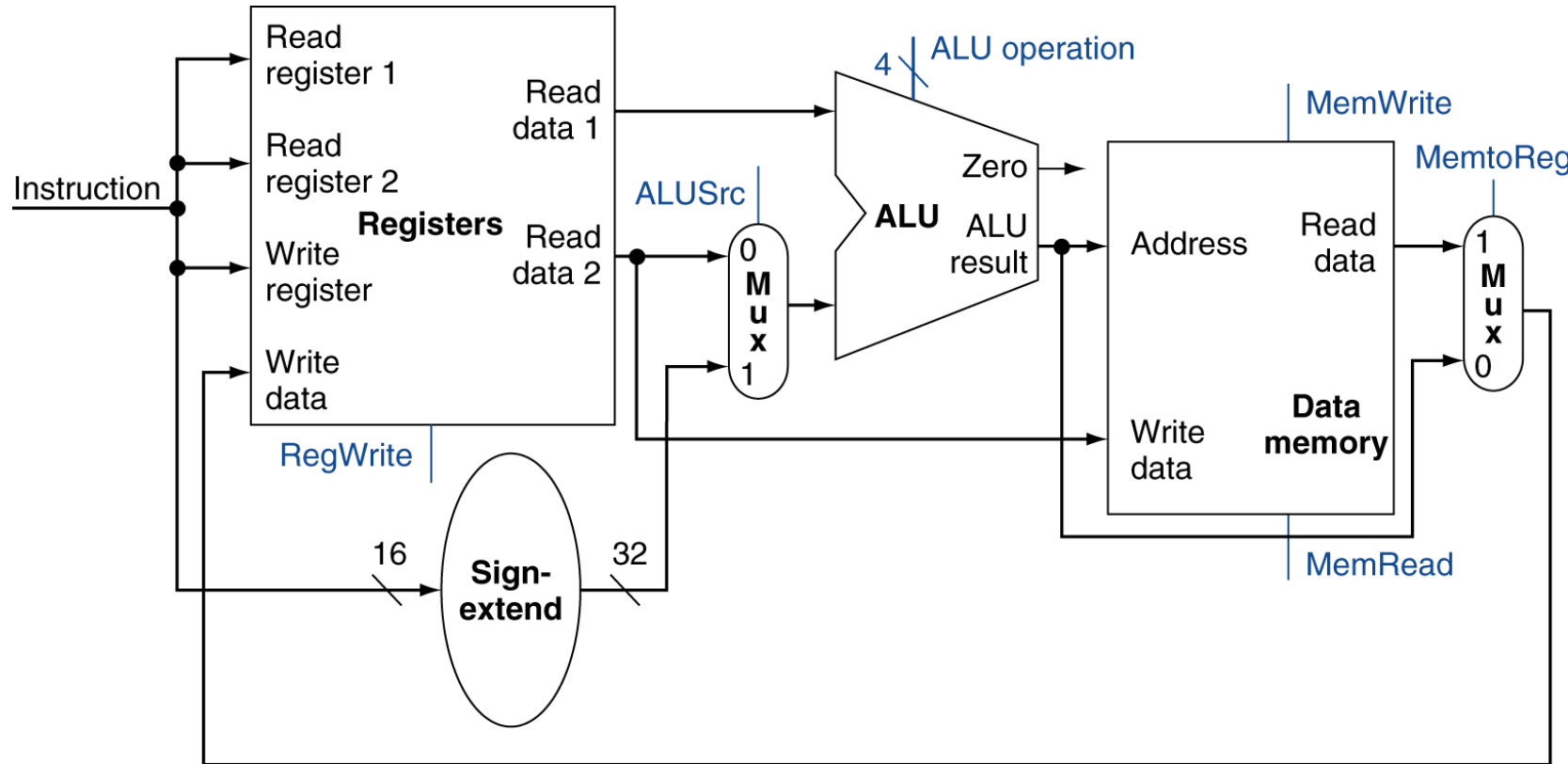\$t0 is register 8, \$t1 is register 9
\$t0 holds 0x07AB8110
0x07AB8114 holds 12



op = lw	rs = 8	rt = 9	imm = 4
---------	--------	--------	---------

Branch Instructions

- Read register operands
- Compare operands
 - Use ALU, subtract and check Zero output
- Calculate target address
 - Sign-extend offset
 - Shift left 2 bits (word offset)
 - Add to PC + 4
 - Already calculated during instruction fetch

Conditional Branch Instructions Require

beq \$t2, \$t3, 0x4F35


A. ALU

B. Registers and an ALU

C. Registers, ALU and Memory

D. Registers, an ALU and an Adder

4. PC-relative addressing

 

Read register operands

Compare operands

Use ALU, subtract and check Zero output

Calculate target address


Sign-extend offset

Shift left 2 bits (word offset)

Add to PC + 4

Already calculated during instruction fetch


Branch Instructions

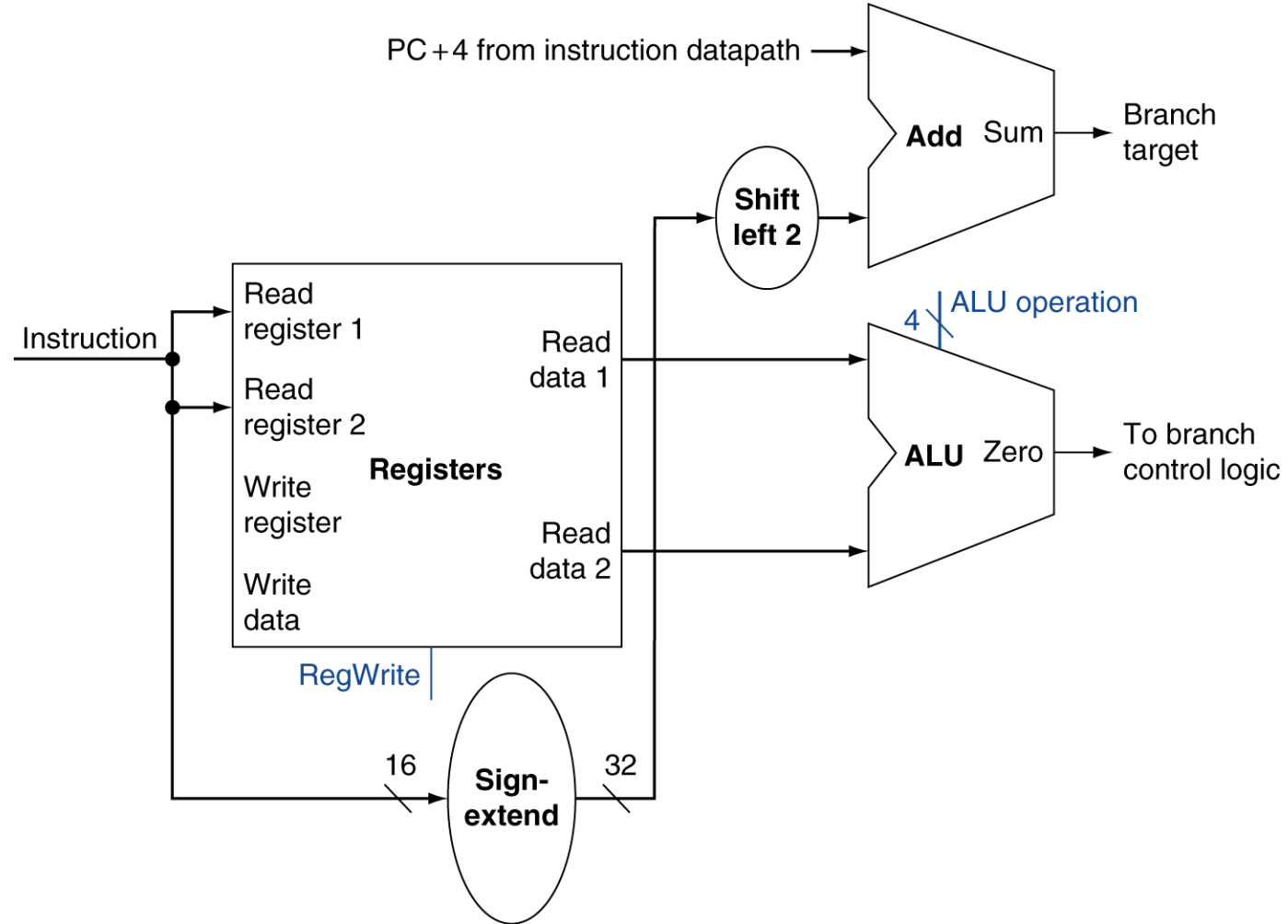

Branch Instructions

0x4045A130 label: add
 0x4045A134 addi
 0x4045A138 beq

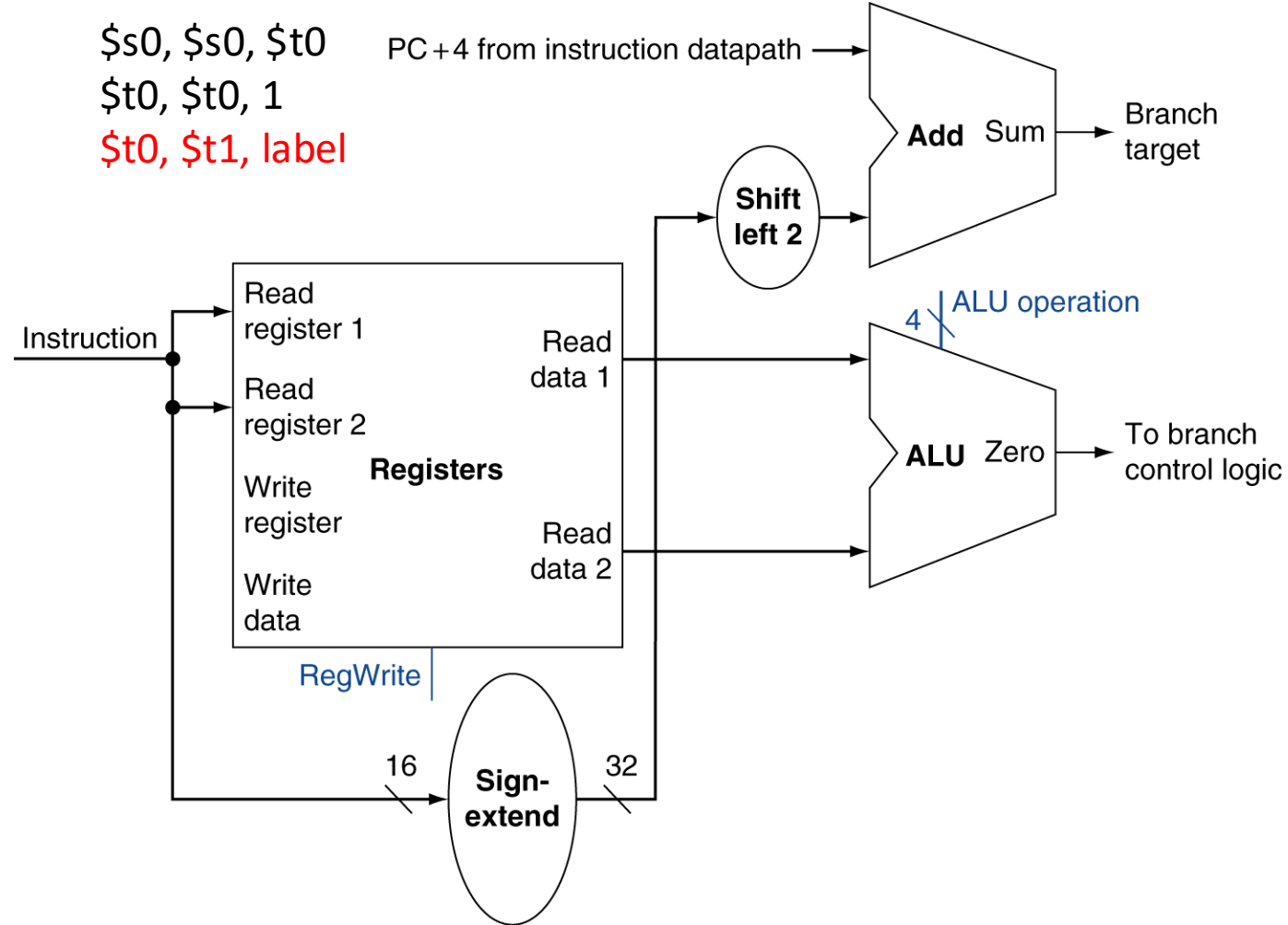
\$s0, \$s0, \$t0 PC+4 from instruction datapath
 \$t0, \$t0, 1
 \$t0, \$t1, label




op = 0x04	rs = 8	rt = 9	imm = 0xFFFFD
-----------	--------	--------	---------------

\$t0 holds 5
 \$t1 holds 5

Datapath (still simplified a bit)

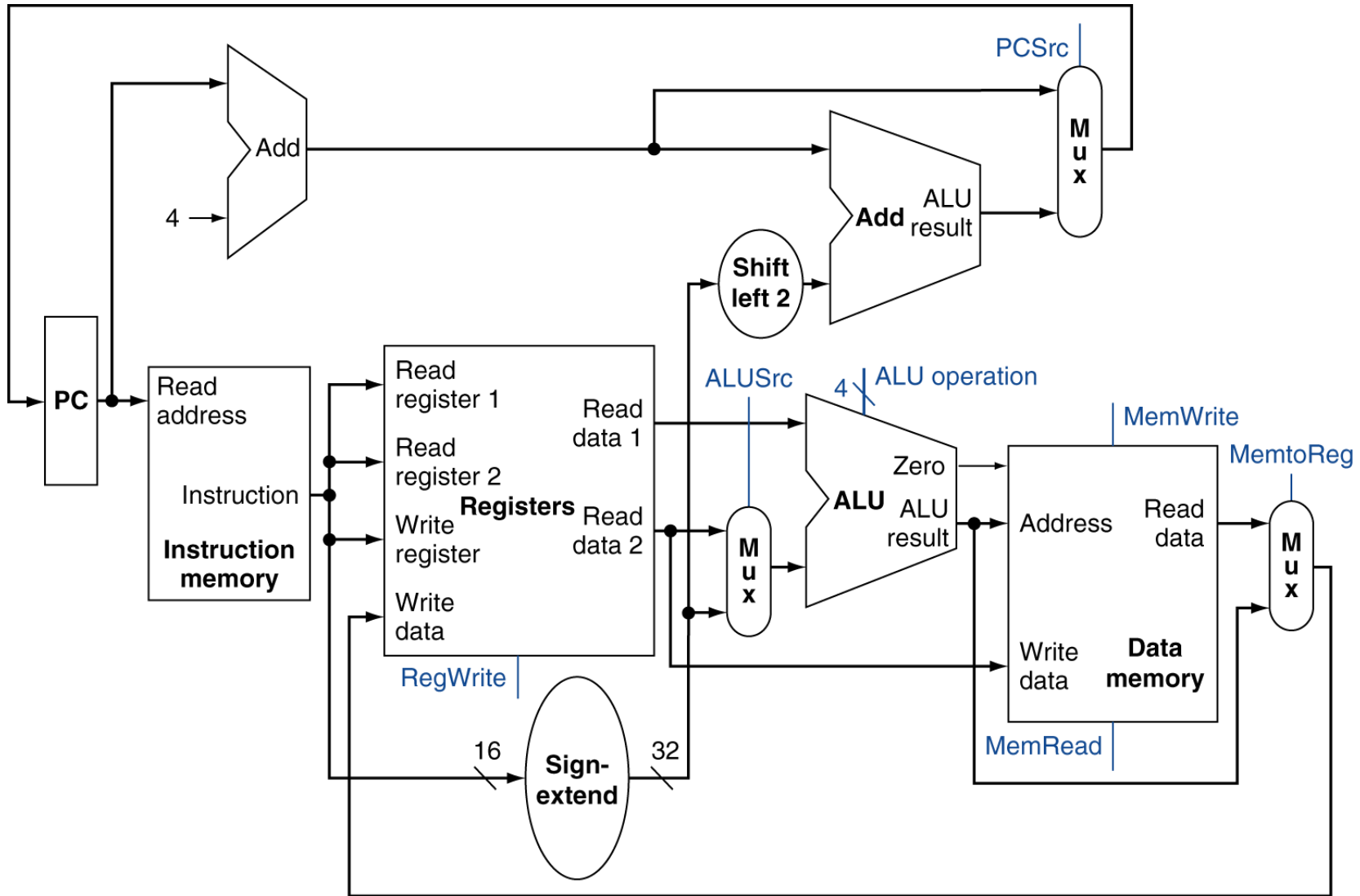


addi \$t1, \$t0, -1

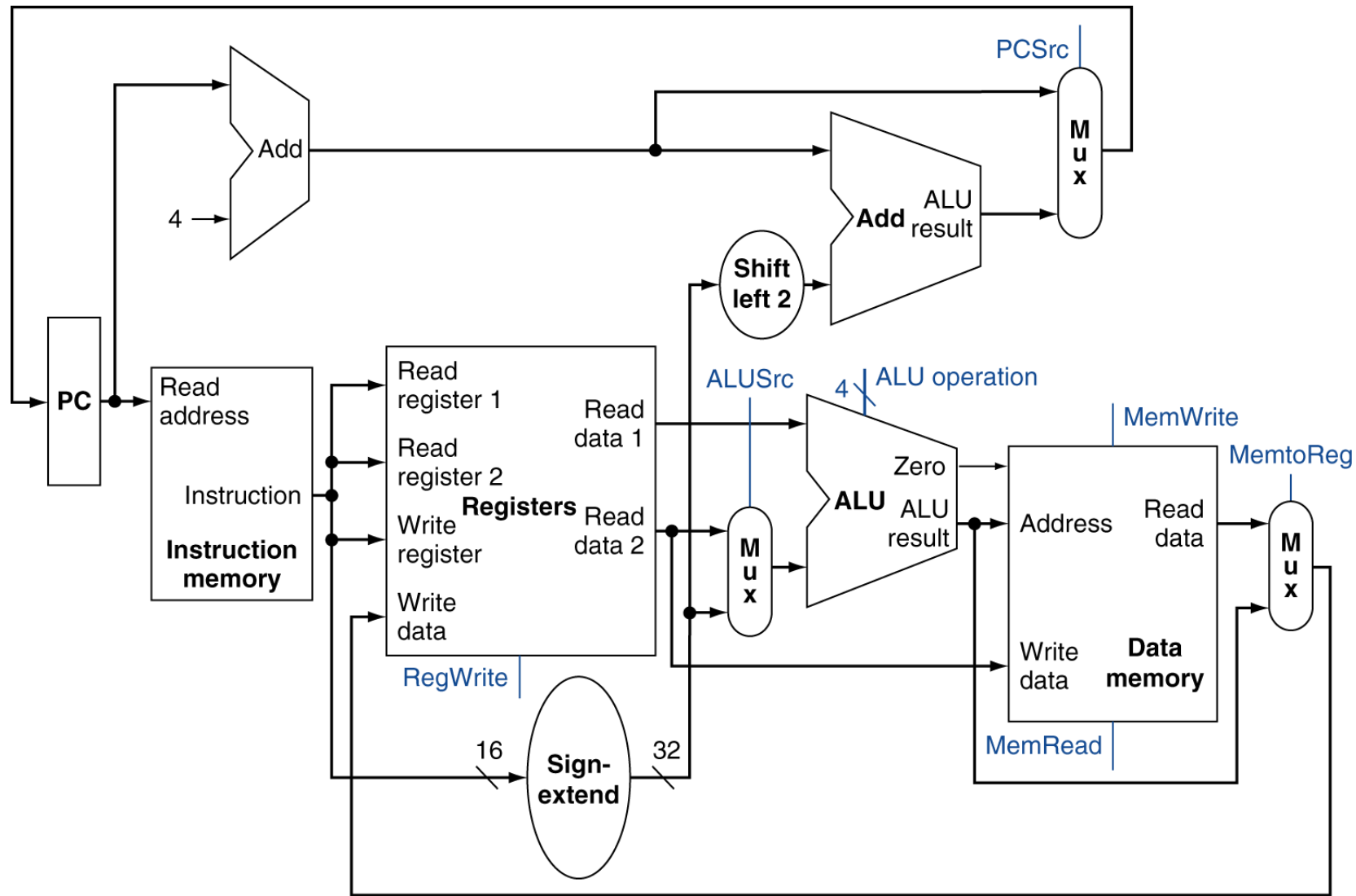

\$t0 holds 10

op = 0x08	rs = 8	rt = 9	imm = 0xFFFF
-----------	--------	--------	--------------

What do we need to add to support ori?

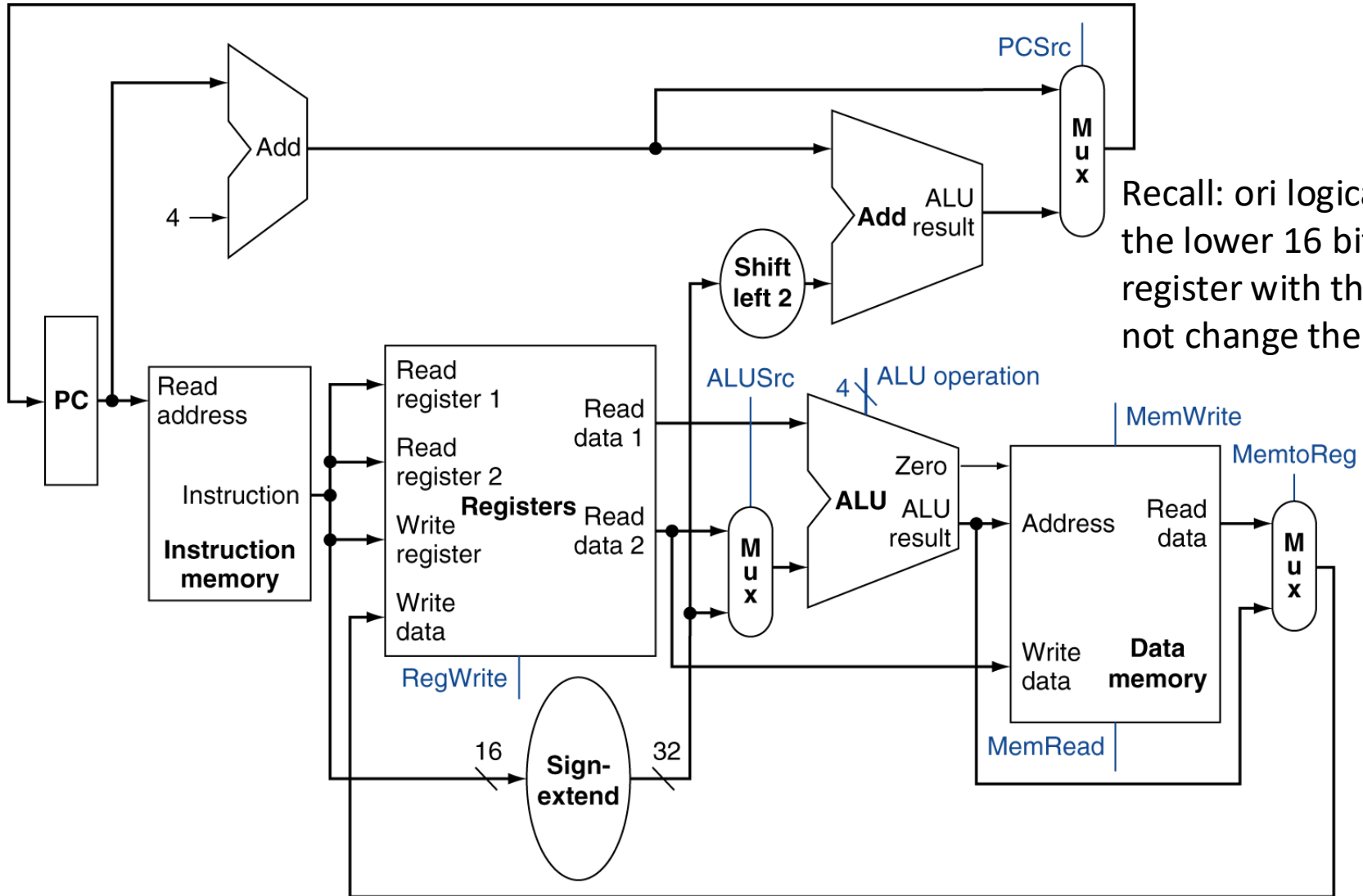


Recall: ori logically ors the lower 16 bits of the specified register with the immediate. It does not change the upper 16 bits.

ori \$t0, \$t1, -3
\$t1 holds 5

op = 0x0D	rs = 9	rt = 8	imm = 0xFFFF
-----------	--------	--------	--------------

sw \$t1, 8(\$t0)

 

\$t0 holds 0x07AB8110

\$t1 holds 5

op = 0x2B	rs = 8	rt = 9	imm = 0x0008
-----------	--------	--------	--------------

Composing the Elements

- Data path does an instruction in one clock cycle
 - Each data path element can only do one function at a time
 - Hence, we need separate instruction and data memories, ALU and adders, etc
- Use multiplexers where alternative data sources are used for different instructions

Key Points

- CPU is just a collection of state and combinational logic
- We just designed a very rich processor, at least in terms of functionality
- $ET = IC * CPI * \text{Cycle Time}$

Reading

- Next lecture: Control Path
 - Section 5.4