
CSCI 210: Computer Architecture

Lecture 19: Clocks, Latches, and Flip Flops

Stephen Checkoway
Slides from Cynthia Taylor


CS History: Latches

 

A Colossus Mark 2 codebreaking computer being operated by Dorothy Du Boisson (left) and Elsie Booker (right), 1943


- The first electronic latch was invented in 1918 by British physicists William Eccles and F. W. Jordan.
- Used in the 1943 British Colossus codebreaking computer (made out of vacuum tubes)
- Modern flip flops made of logic gates were first discussed in a 1954 UCLA course on computer design by Montgomery Phister

S-R Latch

 

- Set (S=1, R=0): $Q_{next} = 1$
- Reset (S=0, R=1): $Q_{next} = 0$
- Neither (S=0, R=0): $Q_{next} = Q_{curi}$

Clock

 

- Oscillates between 1 and 0 with a fixed period
 - 0 to 1 transition is a rising edge
 - 1 to 0 transition is a falling edge
 - Time between two rising (or falling) edges is one period or cycle
- Used to control when values change

Clocked SR Latch


 



Figure 3-23. A clocked SR latch.

  Only changes state when the clock is asserted (meaning the clock has value 1)




D. None of the above

Why Clock a Latch?

 


- Can save the results of combinational logic (think the ALU)
- If a latch is clocked, we know the values in it won't change as we perform combinational logic on them
 - Think of performing addi \$t0, \$t0, 1
- In today's class, we'll build memory that only changes values at one precise instant

Clocked D-Latch

 

- S-R latch, but now there is a single input, D, ANDed with the clock C
- Now impossible to have both inputs set to 1

Which Column Completes the Truth Table?

 


С	D	Q _{next}
1	1	
1	0	

Α	В	С	D
1	1	0	1
1	0	1	Q_{curr}

E. None of the above

Which Column Completes the Truth Table?

 


С	D	Q _{next}
0	1	
0	0	

Α	В	C	D
0	1	1	Q_{curr}
0	0	Q_{curr}	Q_{curr}

E. None of the above


Clocked D-Latch

 


• Latch is "open" when clock is asserted (asserted = logical 1)

Q = value of D when the latch is open
 Q = most recently set value when the latch is closed

 Clocked D-Latch; note output takes a little time to change after the clock goes high



D Flip-Flop

 

• Two D-Latches, with the clock negated to the second latch

The value of (the right-most) Q in the flip flop can change


A. Any time the clock is 1.


B. Any time the clock is 0.




D. When the clock changes from 0 to 1.

E. None of the above

 


 

D flip flop: Falling Edge Trigger

 


Edge-triggering

 

• All changes to state happen at one point in the clock cycle (either rising edge or falling edge).

Memory

 


• Can save the results of combinational logic (think the ALU)


Registers are (multi-bit) flip-flops!

Registers

 Each 32-bit register will consist of 32 1-bit D flip-flops




Register File

 


- Set of registers that can be written/read by supplying a register number
- MIPS has a register file with thirty-two 32-bit registers

Read two register values

 

Write one register value

 

*The image is not quite correct. It should be a lg n to n decoder

In MIPS, we have 32 registers so we need a 5-to-32 decoder, not a 32-to-4294967296 decoder!


What will happen if we read and write to a register in the same clock cycle, as in add \$t0, \$t0, \$s0

A. The read will get the original value

B. The read will get the just written value

C. It is ambiguous

D. None of the above

 

Register Questions


Speed of Combinational Circuits

 Assume each gate takes a certain amount of time for the signal to pass through.

• Gate Delay is measured by counting the number of gates along a path.

Note that all non-sequential gates operate in parallel

 What is the gate delay to calculate carry-out with this circuit?



A. 1

B. 2

C. 3

D. 4

E. None of the above

Minimum clock cycle length

- Minimum clock cycle length is determined by
 - The gate delay of the combinational logic
 - The propagation delay of the flip flop (how long does it take for the output to appear after the flip flop's state is changed)
 - The setup time for the flip flop (how long does the value have to be stable before the falling edge of the clock (for falling edge-triggered flip flops)