

# CSCI 210: Computer Architecture

## Lecture 14: Digital Logic

Stephen Checkoway

Slides from Cynthia Taylor

# CS History: The Manchester Transistor Computer

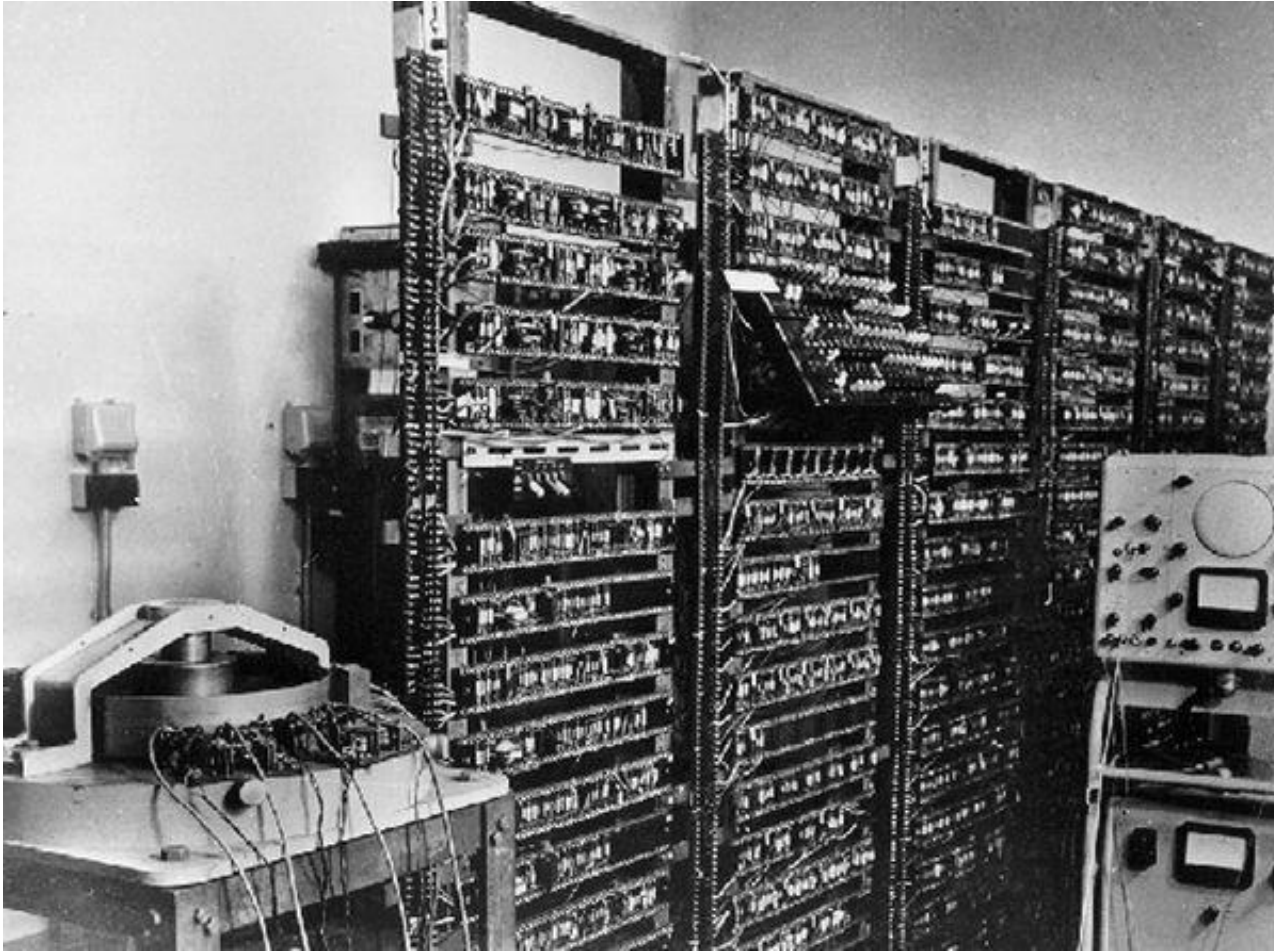



Image credit: The University of Manchester

- First computer to use transistors
- Developed at University of Manchester in 1953
- Problems with the reliability of early batches of transistors meant that its mean time between failures was about 90 minutes
- Still used valves for its clock and memory, so not fully transistorized

# Creating the Universe from 1 and 0

- We have seen how to build programs from assembly
- Now we'll learn how we implement assembly language instructions using circuits

# Machine Interpretation

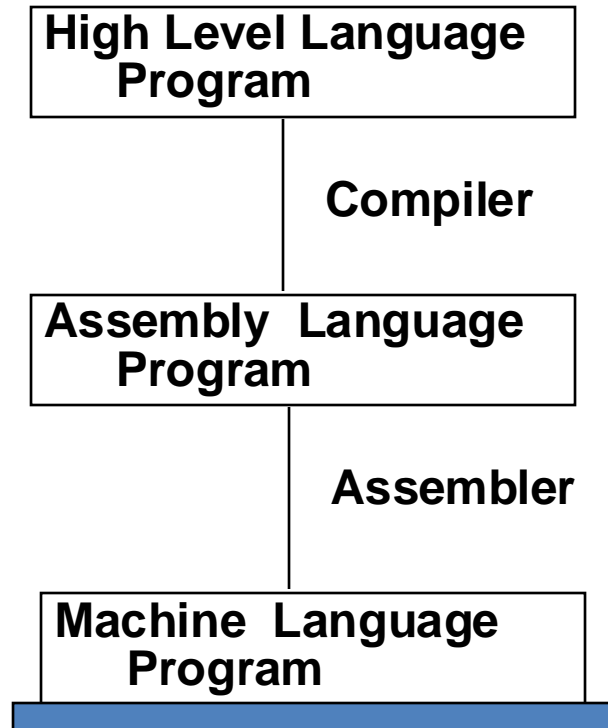

```
temp = v[k];  
v[k] = v[k+1];  
v[k+1] = temp;
```

```
lw $15, 0($2)  
lw $16, 4($2)  
sw $16, 0($2)  
sw $15, 4($2)
```

```
10001100011000100000000000000000  
10001100111100100000000000000100  
10101100111100100000000000000000  
10101100011000100000000000000100
```

**Machine Interpretation**


**Machine does something!**

# A digital circuit is comprised of signals, gates, and wires

- Signals
  - Voltages applied to wires which generate electric current
- Binary signals are represented by different voltages:
  - 0: 0-1 volts
  - 1: 2-5 volts

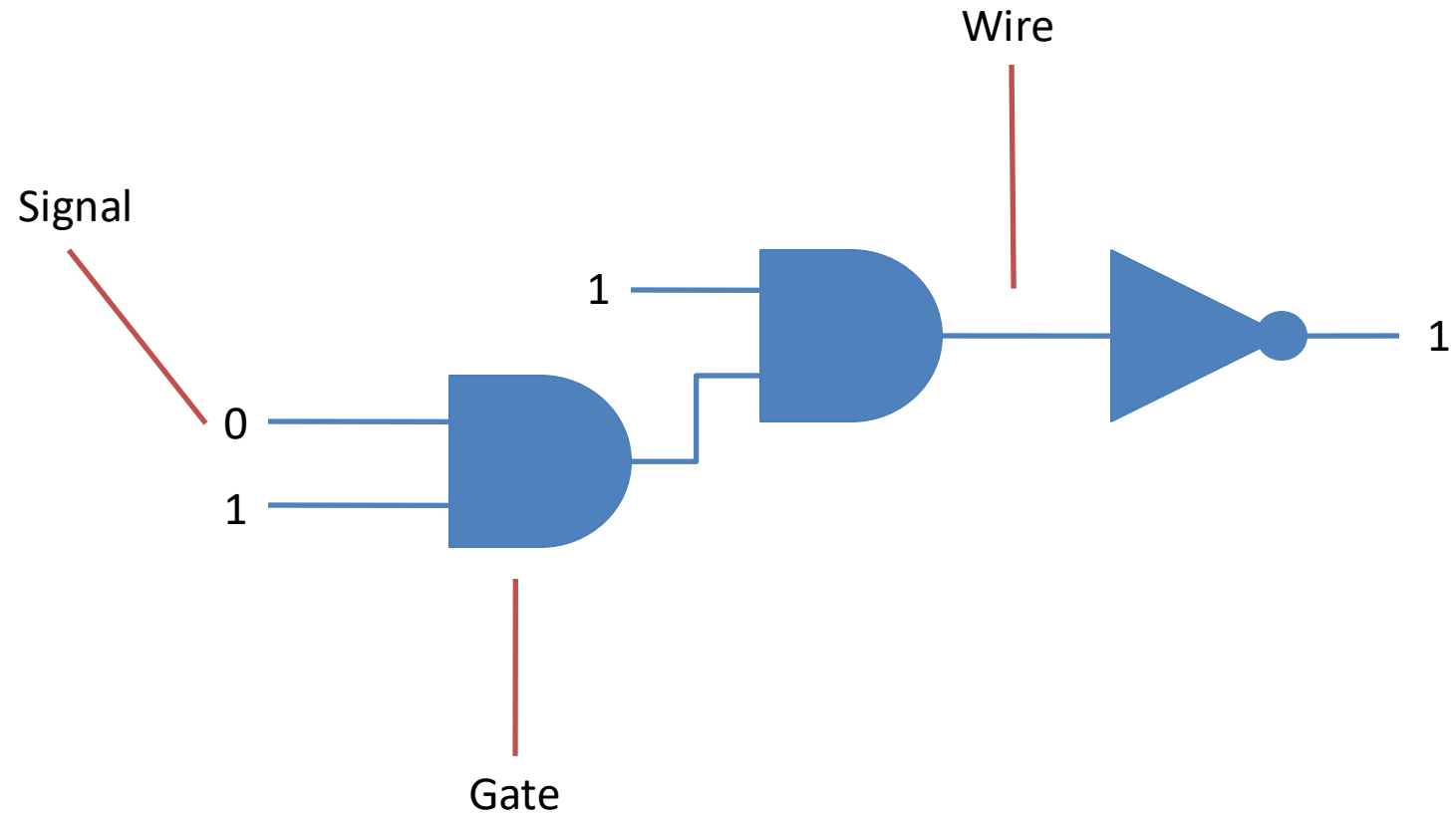
# A digital circuit is comprised of signals, gates, and wires

- Gates
  - Devices which perform operations on signals corresponding to basic logic operations: and, or, not, nand, nor, xor
  - Made out of transistors
- Wires
  - Lines over which signals are transmitted between gates



# Representation of Logic Gates

- Symbol

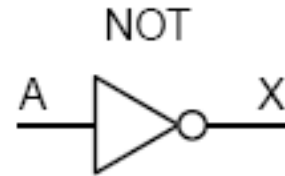

- Truth Table


A	X
0	1
1	0

- Algebraic Representation

$\bar{A}$




# Not

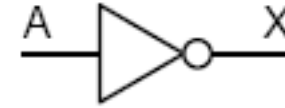

A	X
0	1
1	0

- Inverts the input
- Algebraic representation:  $\bar{A}$


# And

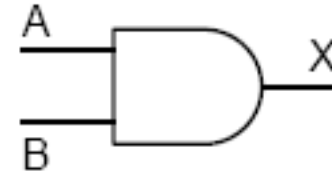

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

- Algebraic representation:  $AB$  or  $A \cdot B$


# Or

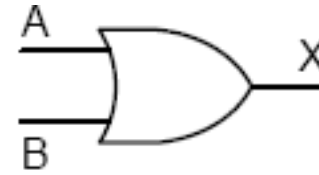

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

- Algebraic representation:  $A+B$


# And and Not

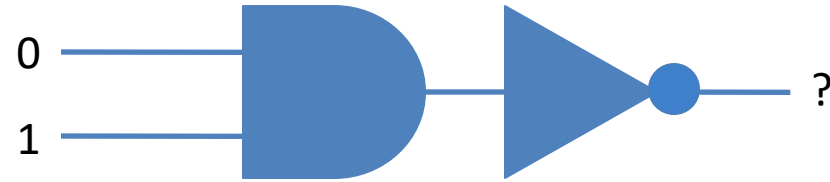

A. 0

B. 1


# Nand

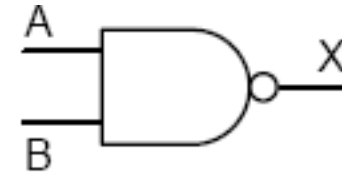

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

- Algebraic representation:  $\overline{(A \cdot B)}$

# Nor

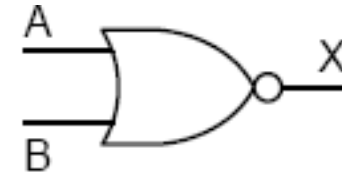

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

- Algebraic representation:  $\overline{(A + B)}$



# Xor



A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

- Algebraic representation:  $A \wedge B$  or  $A \oplus B$

# Our Friend the Transistor

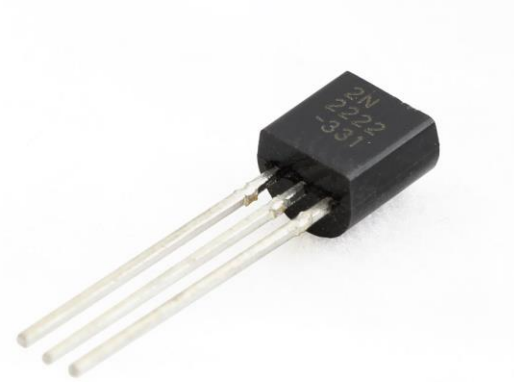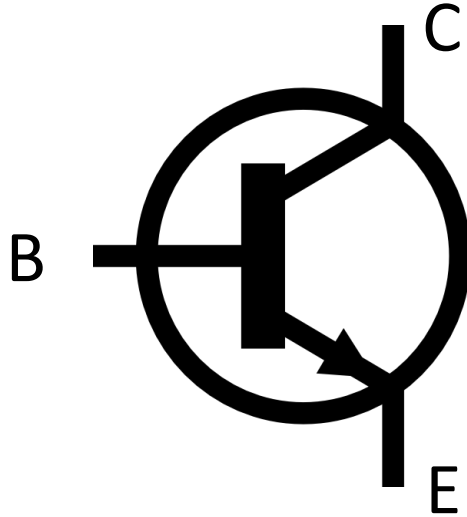


- The basic electronic component from which all gates are created; there are many types, this is an NPN transistor
- Applying a voltage to the base (B) allows current to flow from the collector (C) to the emitter (E)
- This creates an on/off switch


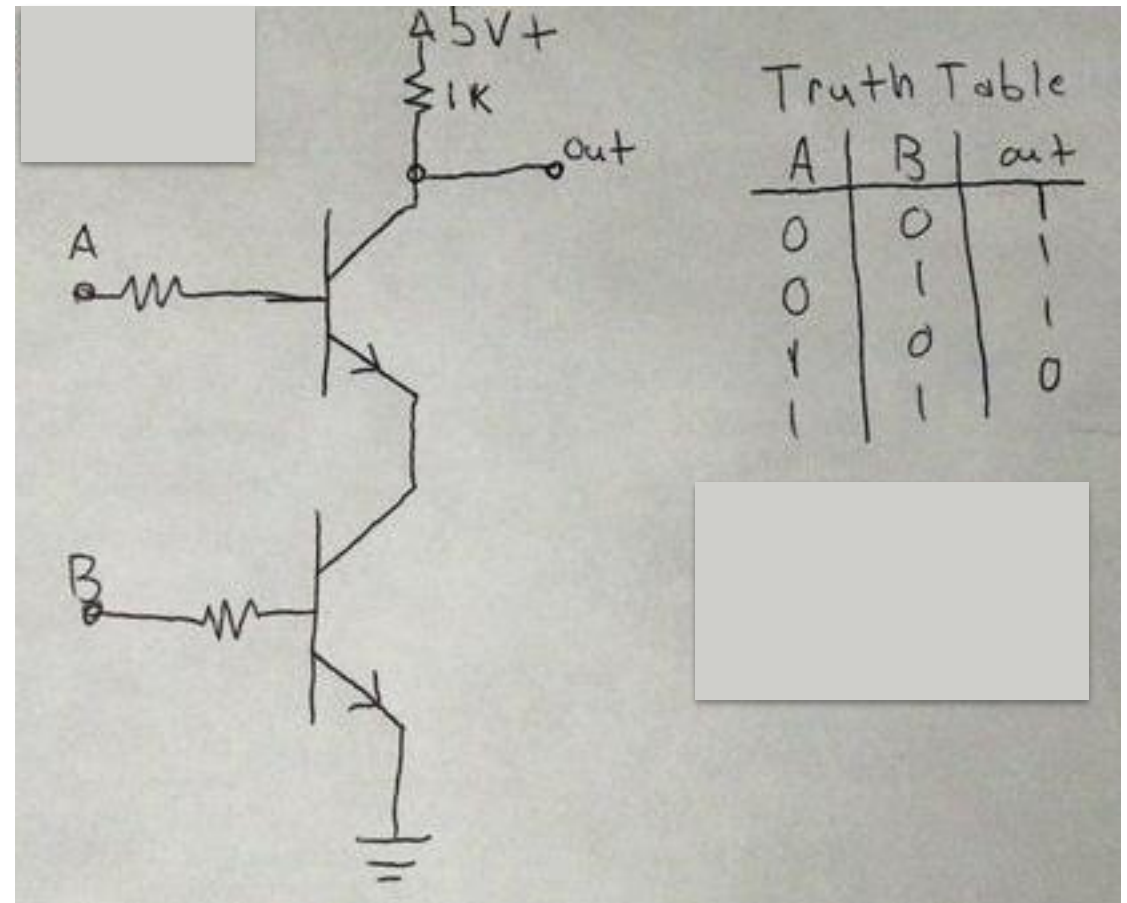
# Building gates out of switches


- Two inputs labeled A and B
- One output labeled out
- When A or B is 1, the other two electrodes (collector and emitter) are connected
- When A and B are both 1, out is connected to ground (logic value 0)
- When either A or B is 0, out is not connected to ground and current can flow from 5V to out




# What Gate Does This Match?

- If both A and B are high voltage (logical 1), out will be low voltage (logical 0)
- Otherwise, out is high voltage

- A. AND
- B. OR
- C. NAND
- D. NOR

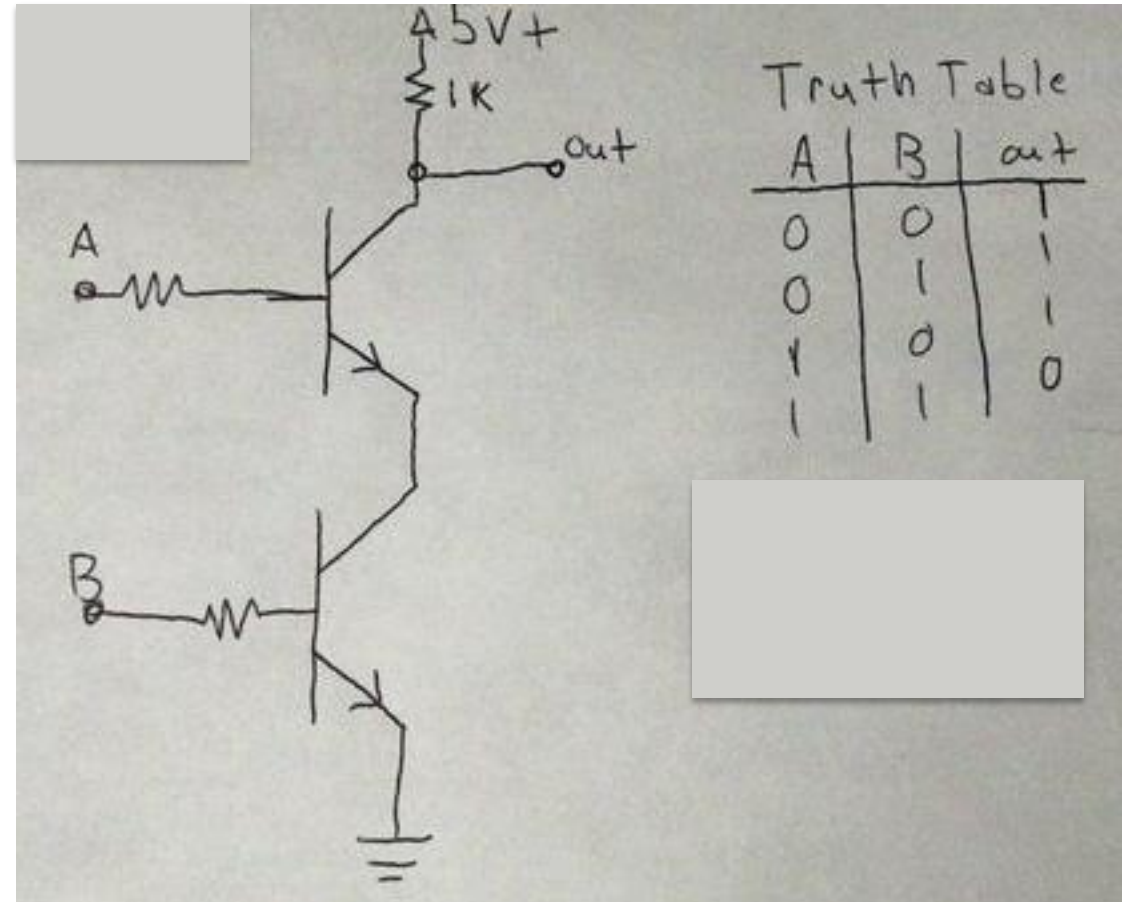

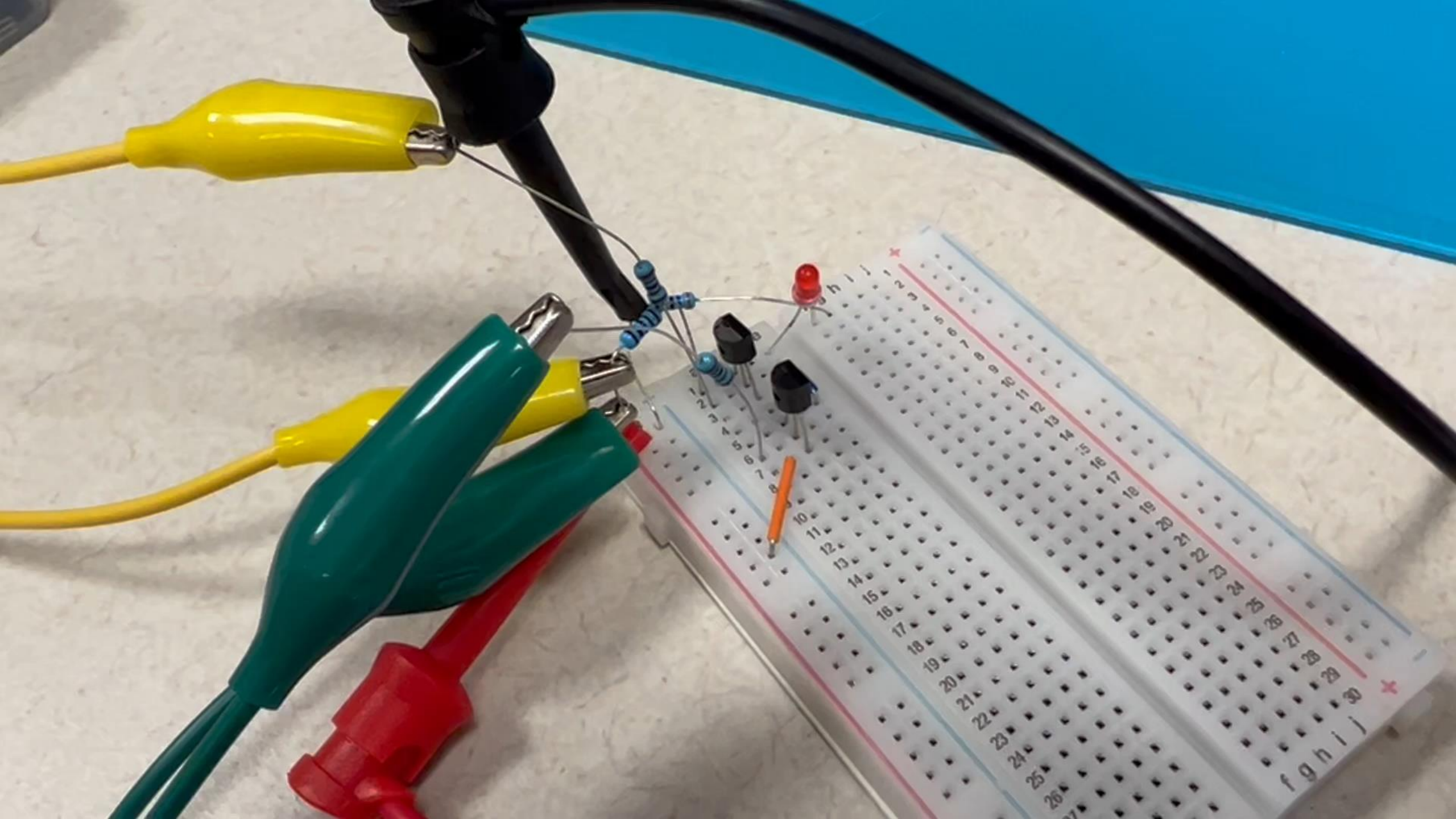

# All Other Gates Can Be Created From NAND



Not

And

# Which is equivalent to A OR B?

- A.  $A \text{ NAND } B$
- B.  $\text{NOT } (A \text{ NAND } B)$
- C.  $(\text{NOT } A) \text{ NAND } (\text{NOT } B)$
- D.  $\text{NOT } ((\text{NOT } A) \text{ NAND } (\text{NOT } B))$
- E. None of the above

# Putting them together

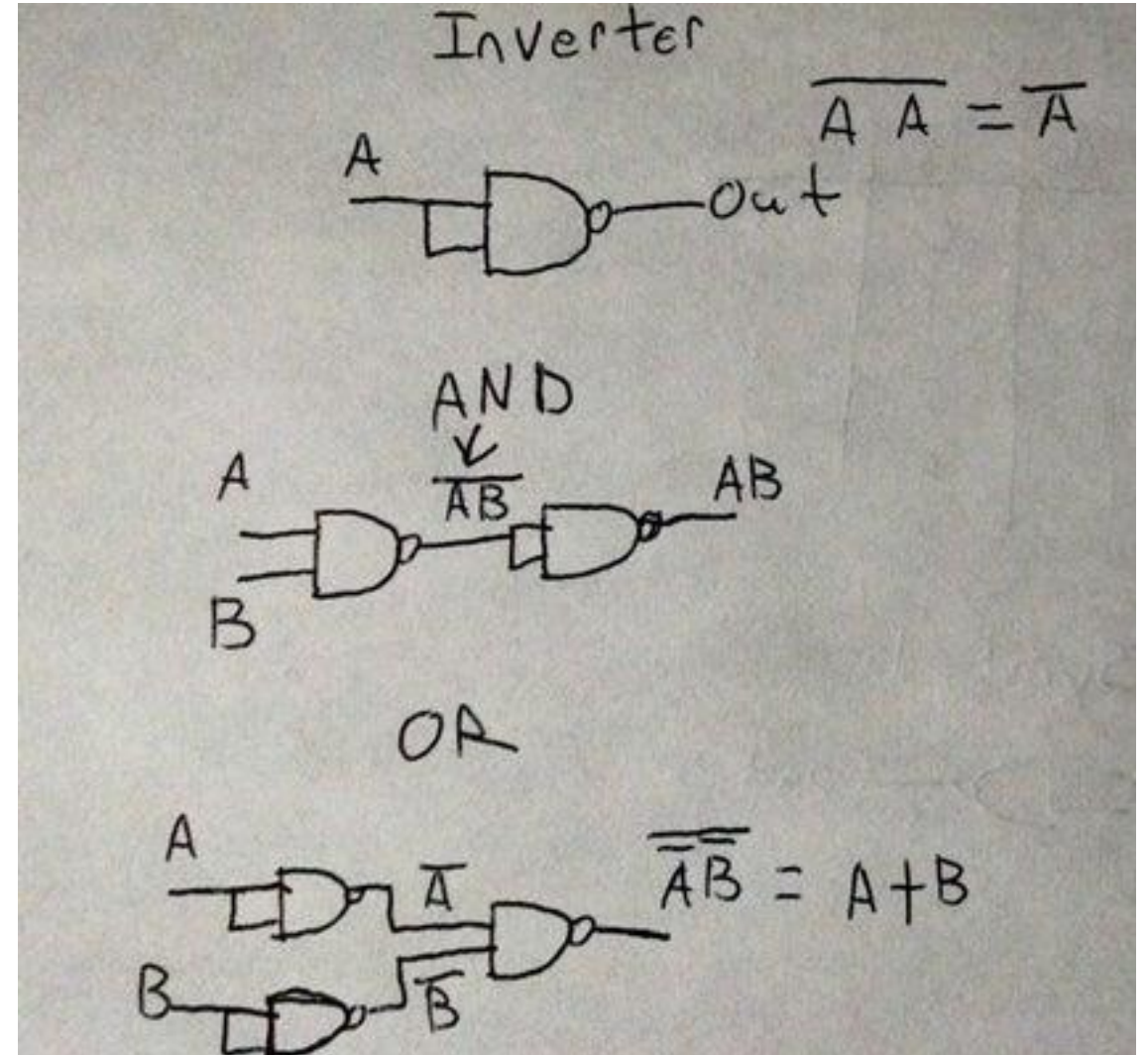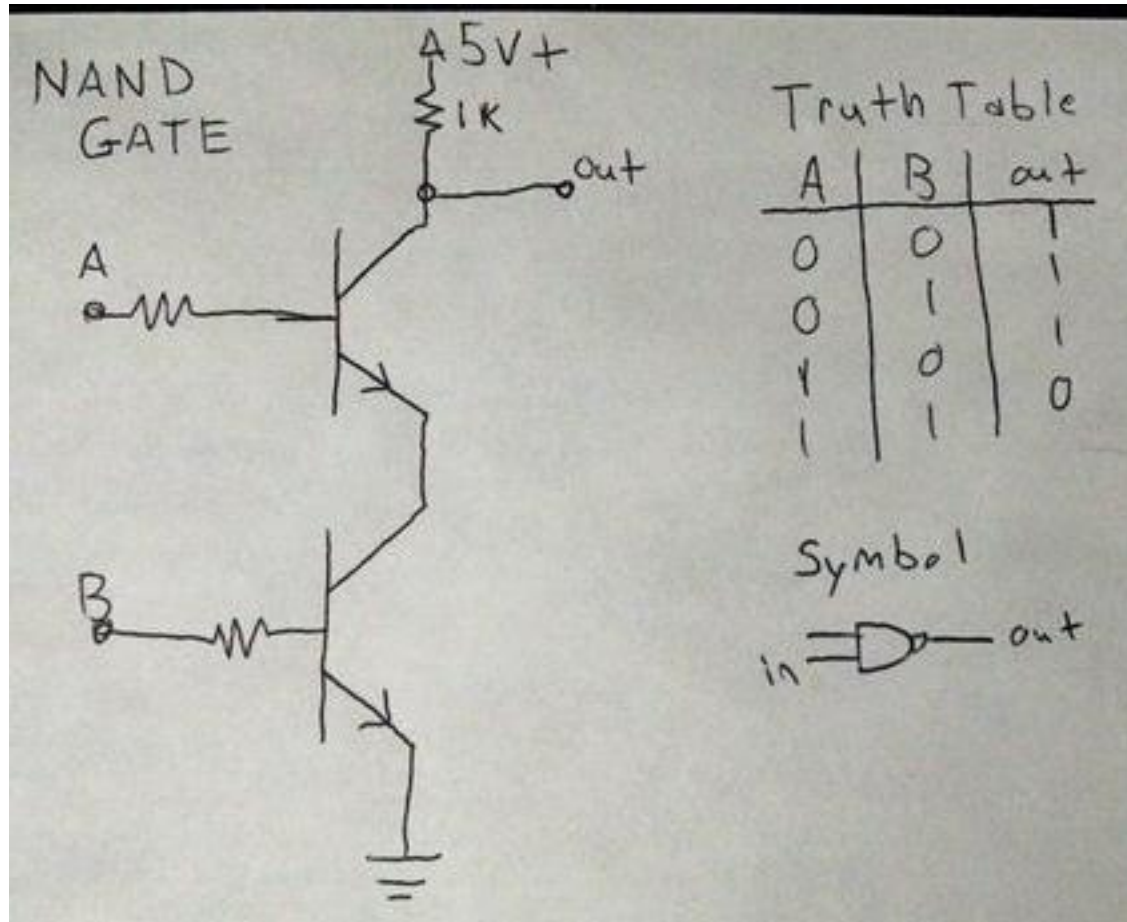

# All Gates Can Also Be Created from NOR

- NOR and NAND are universal gates
  - All gates can be created from them
- You will show this in Problem Set 5

Which column completes the truth table for

$$F = \overline{X} \cdot (Y + Z) ?$$

X	Y	Z	A	B	C	D
0	0	0	0	0	1	1
0	0	1	1	1	1	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	1	0	1	0	1
1	1	0	0	1	0	1
1	1	1	0	1	0	1



Groups: Draw circuit diagram for

$$F = \overline{X} \cdot (Y + Z)$$

$$F = \overline{A} + (B(AC + \overline{AB}))$$

Truth Table

A	B	C	$AC$	$\overline{AB}$	$B(AC + \overline{AB})$	$F$
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

# Reading

- Next lecture: Boolean Algebra
  - 3.3
- Problem Set 4 due Friday
- Lab 3 due Monday