### CSCI 210: Computer Architecture Lecture 26: Control Path

Stephen Checkoway Slides from Cynthia Taylor

# CS History: Apple Lisa



- First mass-market PC that used a graphical user interface
- Released in 1983
- Cost \$9,995 (equivalent to \$29,400 in 2022)
- Used the Motorola 68000 CPU, the first 32-bit CPU
- Shipped with 1 MB of RAM

### **Control Path**

 Our data path is complicated, and we don't use each element every time

• How do we know which elements to use?

### Recall: PLAs



• Derived from truth table using sum of products

• Allow us to encode arbitrary functions

• Used to derive control signals in the data path

#### Datapath With Control



#### The Main Control Unit

#### Control signals derived from instruction opcode



# **Fetching Instructions**

- Read instruction from Instruction Memory
- Updating PC value to address of next (sequential) instruction
- PC is updated every clock cycle, so it does not need an explicit write control signal just a clock signal
- Read from memory each time, so we don't need an explicit control signal





- Read two values from the Register File
- Register numbers are contained in the instruction (rs and rt)

# Producing control signals

After reading opcode

- Produce most control signals
- Includes the ALUOp control signal—which goes to the ALU control unit—and the ALUSrc control signal which selects the ALU's second operand



# For load/store, our ALU operation will be

A. Add

B. And

C. Set less than

D. Subtract

E. None of the above



lw \$t0, 4(\$t1)

# ALU Control Unit

- Combinational logic (the main control unit) derives 2-bit ALUOp signal from opcode
- ALU Control Unit takes ALUOp and instruction funct field as inputs and derives a 4-bit ALU control signal

opcode	ALUOp	Operation	ALU function
lw	00	load word	add
SW	00	store word	add
beq	01	branch equal	subtract
R-type	10	arithmetic/logic	depends on funct





# **ALU Control signal**

- ALU used for
  - Load/Store: op = add
  - Branch: op = subtract
  - R-type: op depends on funct field



ALU control	Function	Ainvert	Binvert/CarryIn0	Operation
0000	AND	0	0	00
0001	OR	0	0	01
<mark>0</mark> 010	add	0	0	10
<mark>0</mark> 110	subtract	0	1	10
<mark>0</mark> 111	set-on-less-than	0	1	11
<b>1</b> 100	NOR	1	1	00

# **ALU Control**



# Takes as input 2-bit ALUop (derived from opcode) and 6-bit funct field; outputs 4 bits

Instruction	ALUOp	funct	ALU function	Ainvert	Binvert	ALU operation
load word	00 (add)	XXXXXX	add	0	0	10 (add)
store word	00 (add)	XXXXXX	add	0	0	10 (add)
branch equal	01 (subtract)	XXXXXX	subtract	0	1	10 (add)
add	10 (r-type)	100000	add	0	0	10 (add)
subtract		100010	subtract	0	1	10 (add)
AND		100100	AND	0	0	00 (and)
OR		100101	OR	0	0	01 (or)
NOR		100111	NOR	1	1	00 (and)
set-on-less-than		101010	set-on-less-than	0	1	11 (less)

#### **Executing R Format Operations**

• R format operations (add, sub, slt, and, or)

	31	25	20	15	10	5 0
R-type:	ор	rs	rt	rd	shamt	funct

- perform operation (specified by funct) on values in rs and rt

- store the result back into the Register File (into location rd)



Note that Register File is not written every cycle (e.g., **sw**), so we need an explicit write control signal for the Register File



#### **R-Type Instruction**



#### **Executing Load and Store Operations**

- compute memory address by adding base register to 16-bit signed-extended offset field
- store value written to the Data Memory
- load value read from the Data Memory, written to the Register File





#### Which wire, if always set to 1 would break lw?



Load/

Store



25:21

20:16

31:26

ALUOp = 00 (add) ALUOp = 01 (subtract) ALUOp = 10 (R-type)





#### **Executing Branch Operations**

- Branch operations involve
  - compare the operands read from the Register File during decode for equality (zero ALU output)
  - compute the branch target address by adding the updated PC to



#### **Branch-on-Equal Instruction**



31:26 25:21 20:16 15:0

### **Control Truth Table**

		R-format	lw	SW	beq
Opcode		000000	100011	101011	000100
	RegDst	1	0	X	X
	ALUSrc	0	1	1	0
Outputs	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1

ALUOp = 00 (add)

ALUOp = 01 (subtract)

ALUOp = 10 (R-type, use funct to determine ALUCtrl signals)

# Implementing Jumps



- Jump uses word address
- Update PC with concatenation of
  - Top 4 bits of PC + 4
  - 26-bit jump address
  - 00



Select	Best Answer
А	Yes – we need both new control and datapath.
В	Yes – we need just datapath.
С	No – but we should for better performance.
D	No – just changing control signals is fine.
Е	Single cycle can't do jump register.

#### Datapath With Jumps Added





