

# CSCI 210: Computer Architecture

## Lecture 29: Pipelining


Stephen Checkoway

Slides from Cynthia Taylor


# CS History: Berkeley RISC

- Developed by David Patterson at UC Berkeley between 1980 and 1984
- Patterson took a sabbatical to improve DEC's Complex Instruction Set, and instead decided the whole system was bad
- A 1978 Andrew Tannenbaum paper had shown a 10,000 line complex program could be implemented using a simplified ISA with an 8-bit fixed opcode
  - And that 81% of constants were 0, 1 or 2!
  - IBM internally discovered similar results
- First RISC chip came out in 1981
- RISC V is currently in active development as an open-source ISA

# Pipelined Datapath

 

# IF for sw \$t0, 4(\$t1)

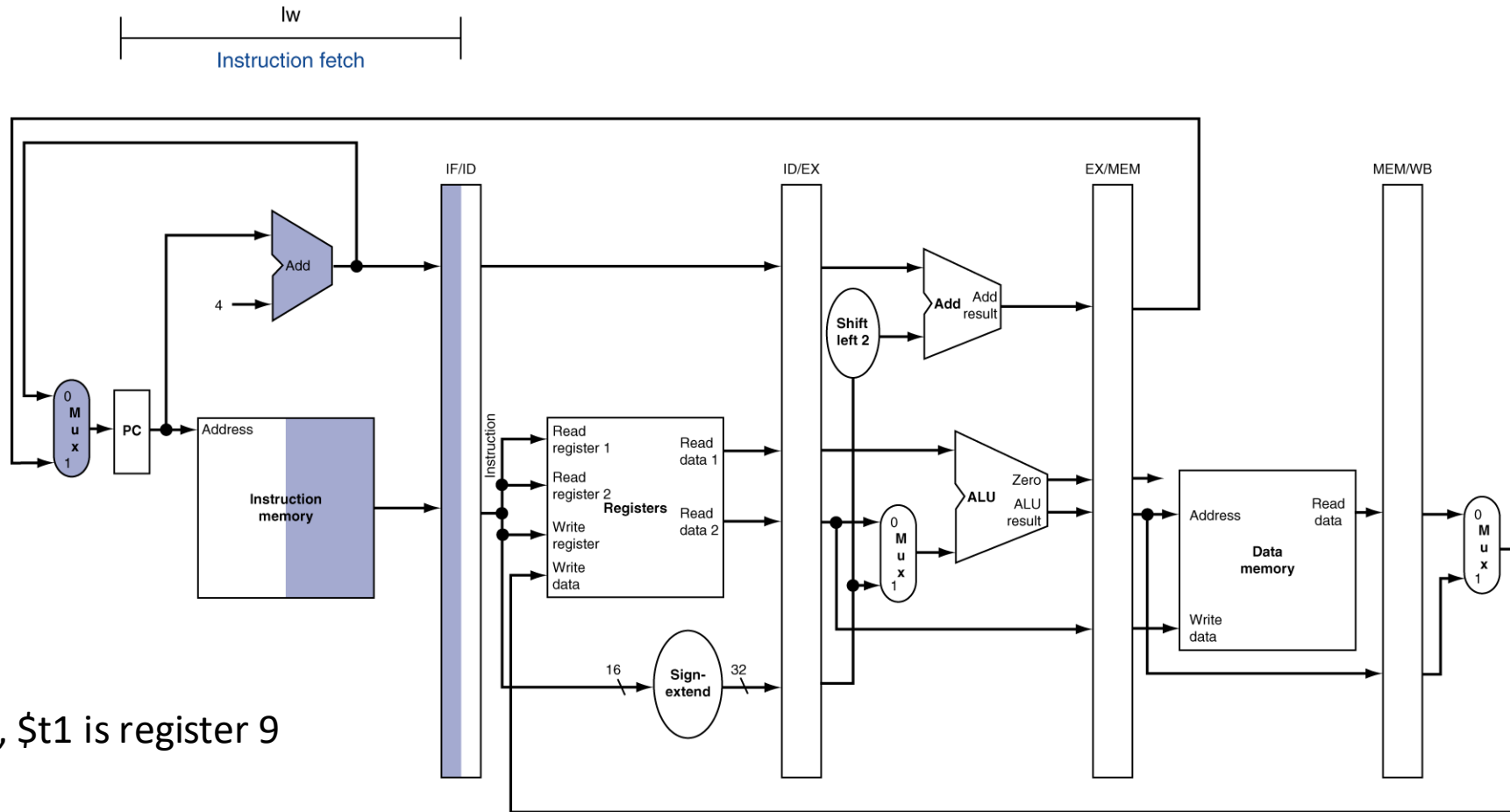


\$t0 is register 8, \$t1 is register 9

\$t0 holds 5

\$t1 holds 0x4810CAB0



0x4810CAB0 holds 12

# ID for sw \$t0, 4(\$t1)

 


\$t0 is register 8, \$t1 is register 9  
\$t0 holds 5  
\$t1 holds 0x4810CAB0  
0x4810CAB0 holds 12

# EX for sw \$t0, 4(\$t1)

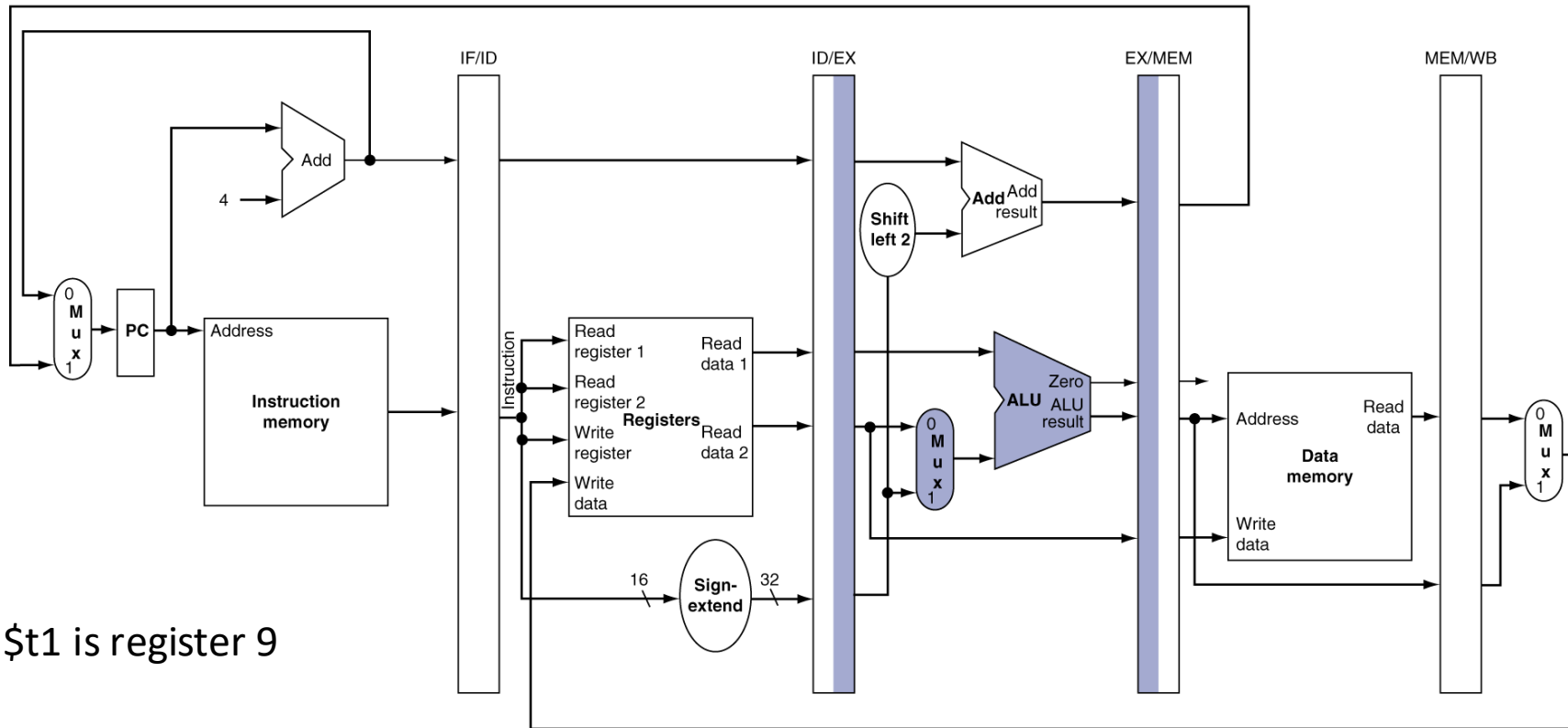 


\$t0 is register 8, \$t1 is register 9  
\$t0 holds 5  
\$t1 holds 0x4810CAB0  
0x4810CAB0 holds 12

# MEM for sw \$t0, 4(\$t1)

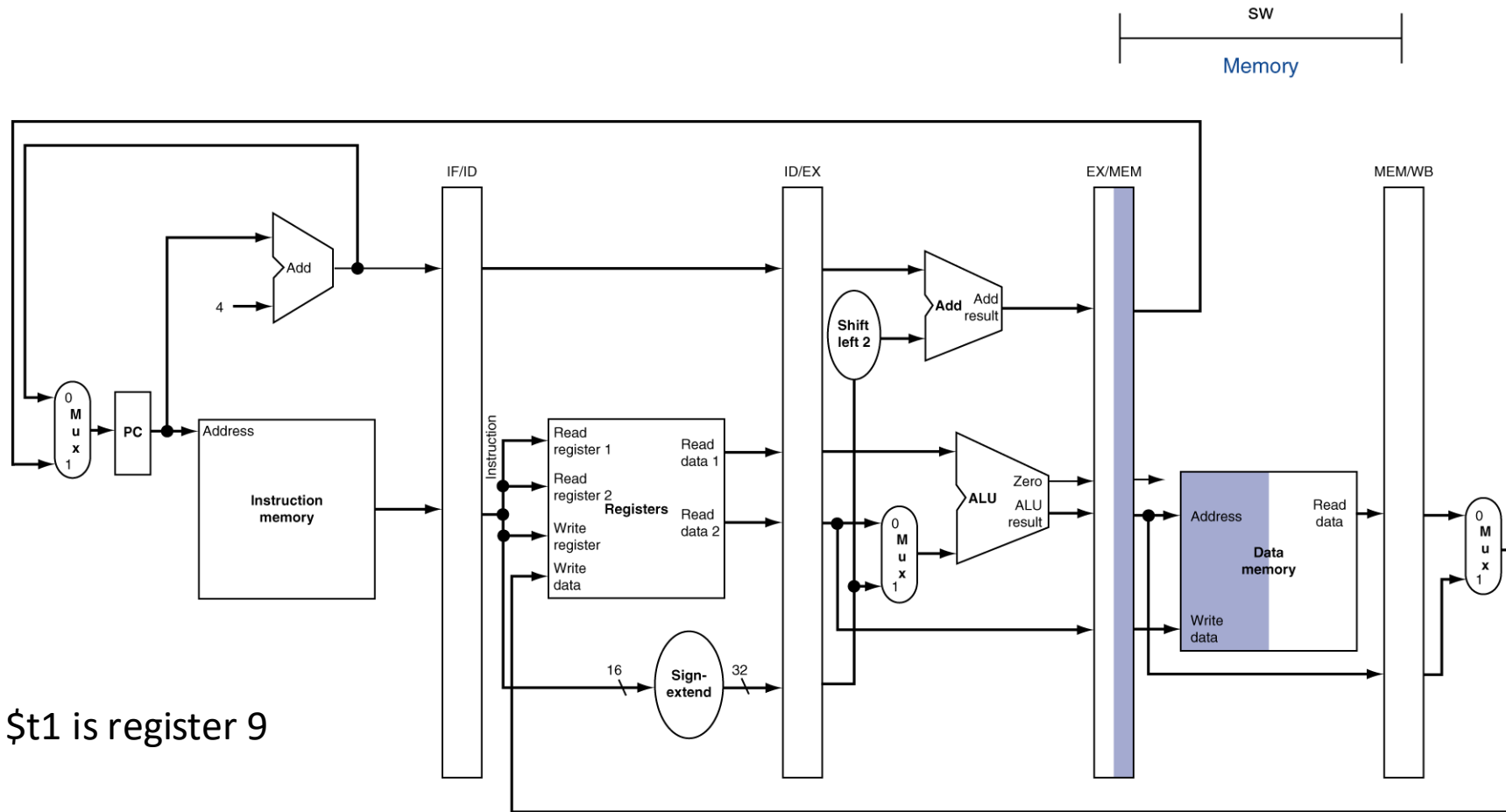

\$t0 is register 8, \$t1 is register 9  
\$t0 holds 5  
\$t1 holds 0x4810CAB0  
0x4810CAB0 holds 12

# WB for sw \$t0, 4(\$t1)

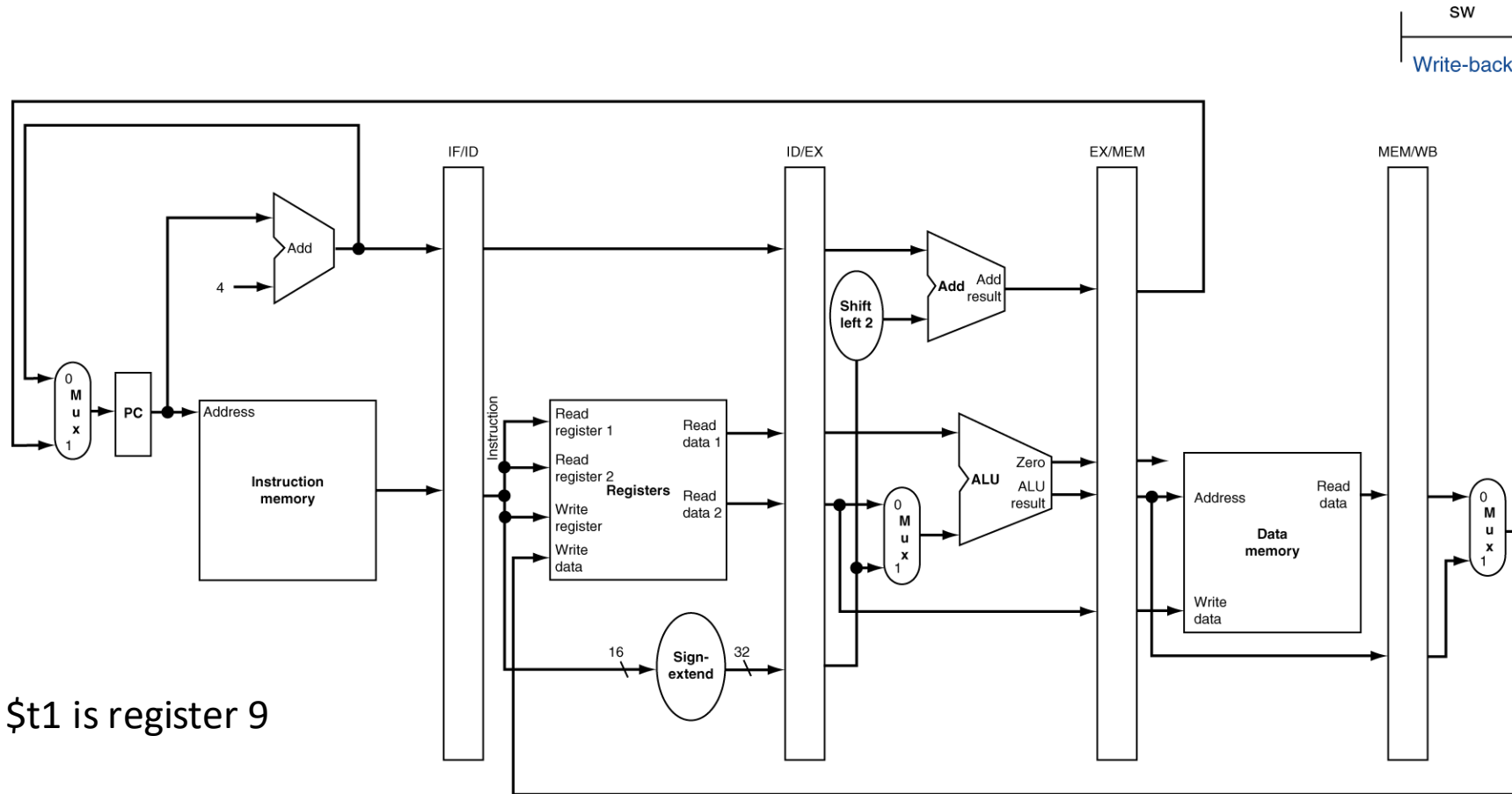

\$t0 is register 8, \$t1 is register 9  
\$t0 holds 5  
\$t1 holds 0x4810CAB0  
0x4810CAB0 holds 12




# Pipeline Stages

Should we force every instruction to go through all 5 stages? Can we break it up, with R-type taking 4 cycles instead of 5?


Selection	Yes/No	Reason (Choose BEST answer)
A	Yes	Decreasing R-type to 4 cycles improves instruction throughput
B	Yes	Decreasing R-type to 4 cycles improves instruction latency
C	No	Decreasing R-type to 4 cycles causes hazards
D	No	Decreasing R-type to 4 cycles causes hazards and doesn't impact throughput
E	No	Decreasing R-type to 4 cycles causes hazards and doesn't impact latency

# Mixed Instructions in the Pipeline

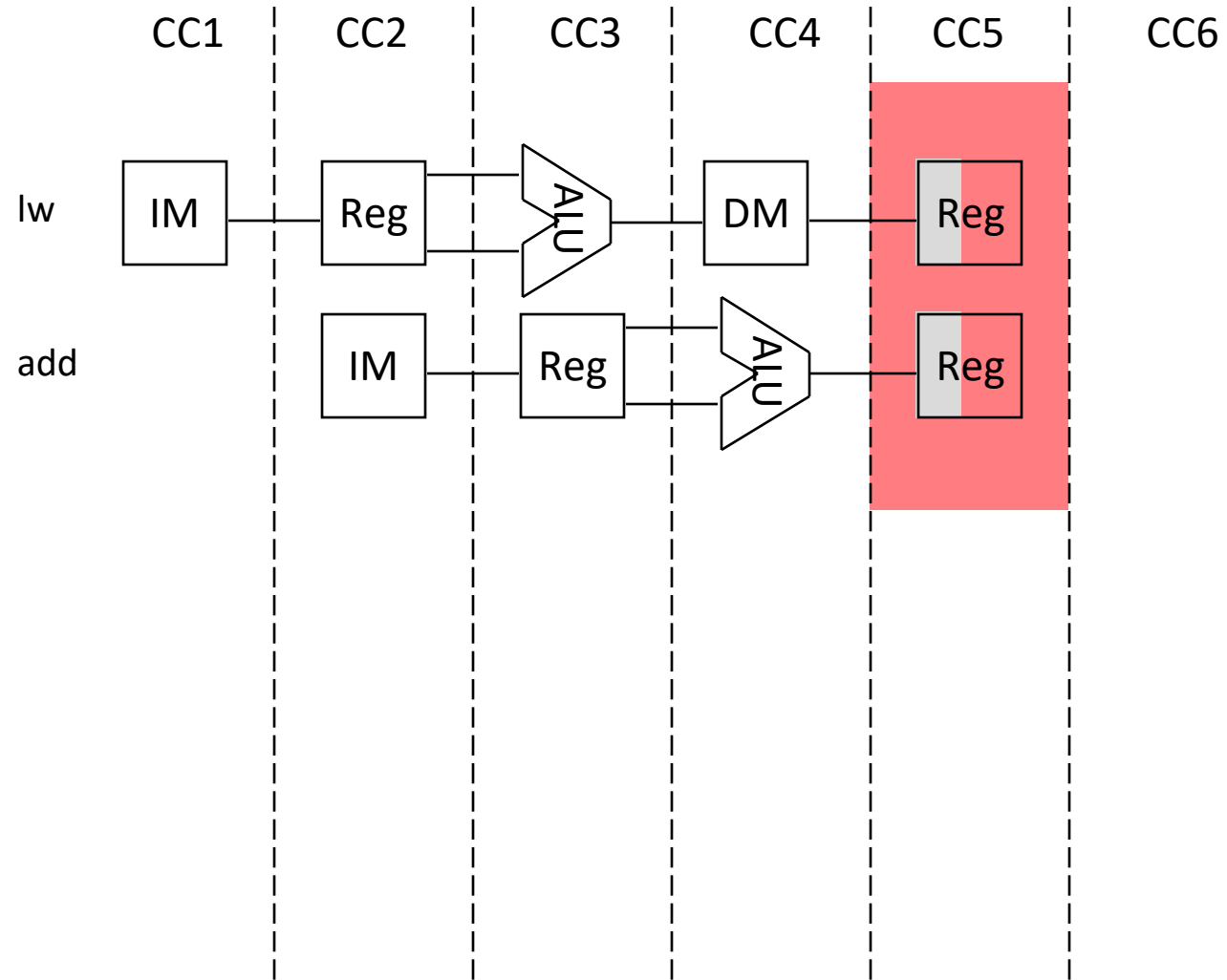


# State of pipeline in a given cycle

add \$14, \$5, \$6	lw \$13, 24 (\$1)	add \$12, \$3, \$4	sub \$11, \$2, \$3	lw \$10, 20(\$1)
Instruction fetch	Instruction decode	Execution	Memory	Write-back

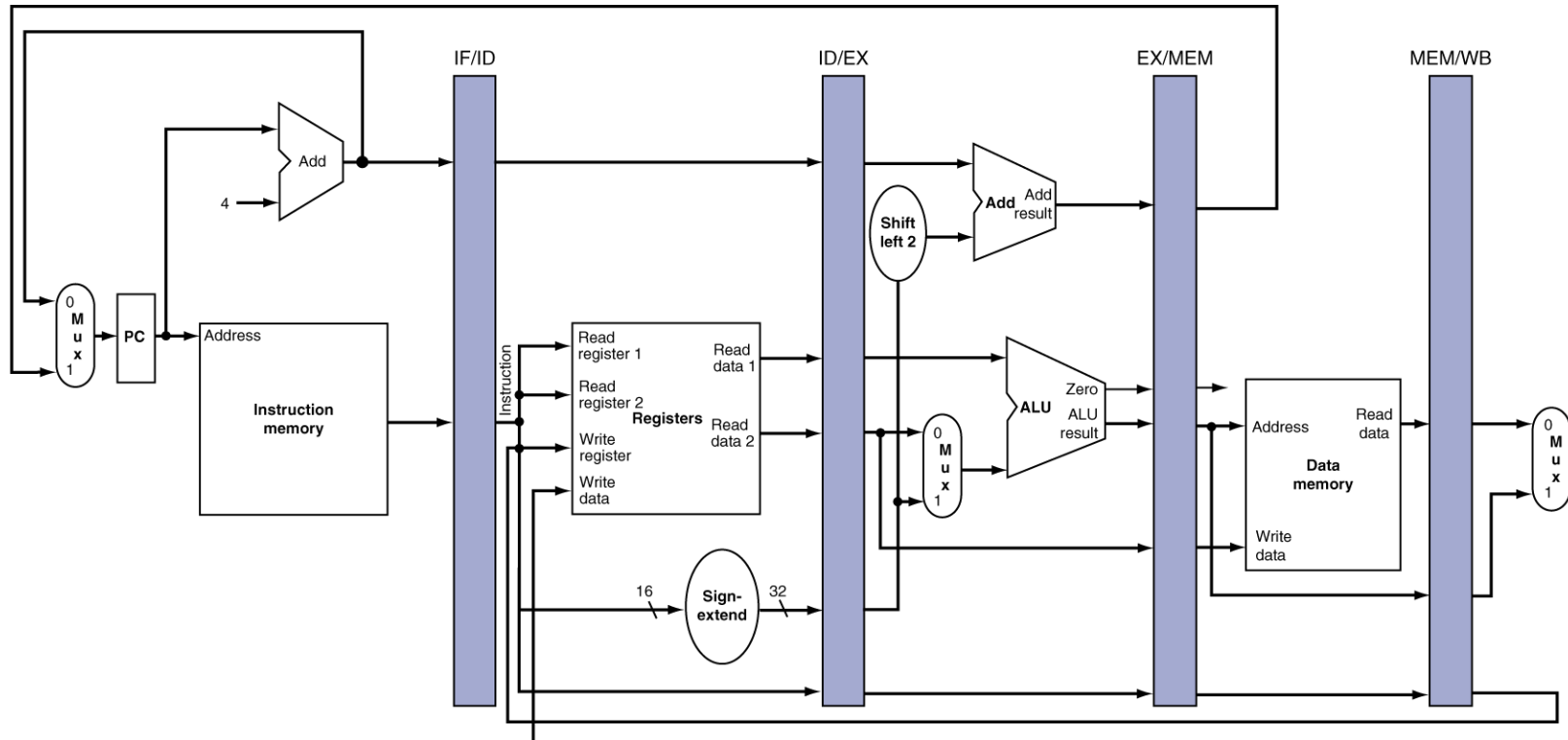

# Pipelined Control

 

# How do we control our pipelined CPU?


- A. We need to add new control signals.
- B. We need to forward the control values to the correct stage.
- C. We don't need to do anything special; it will work the way it is.

# Pipeline Control


- IF Stage: read Instr Memory (always) and write PC (on System Clock)
- ID Stage: no optional control signals to set
- EX, MEM, and WB stages have control signals
  - The pipeline registers will need to store the control signals

# Pipelined Control

Control signals derived from instruction

 

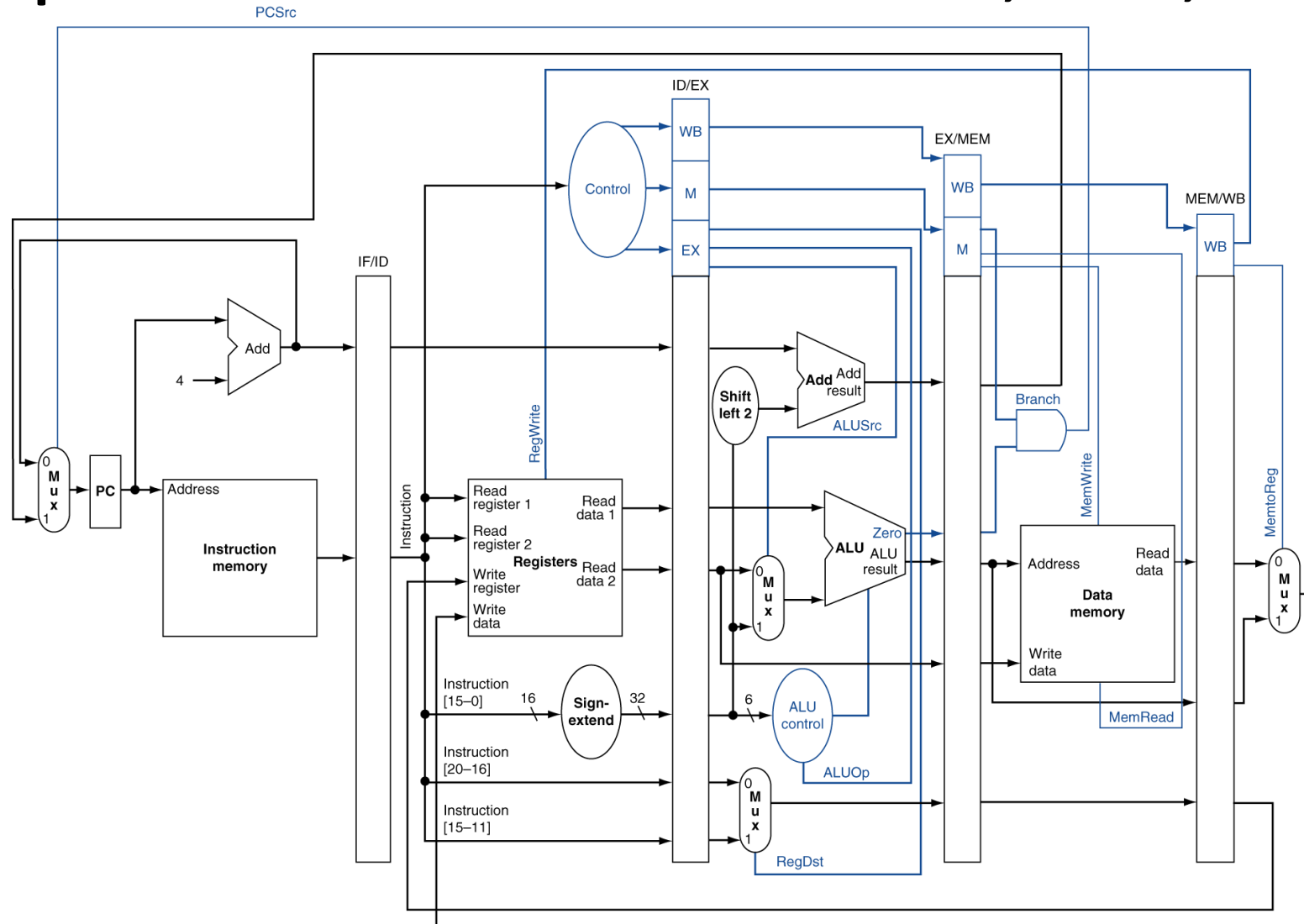
# Pipelined Control: add \$t0, \$t1, \$t2



\$t1 holds 5  
\$t2 holds 6



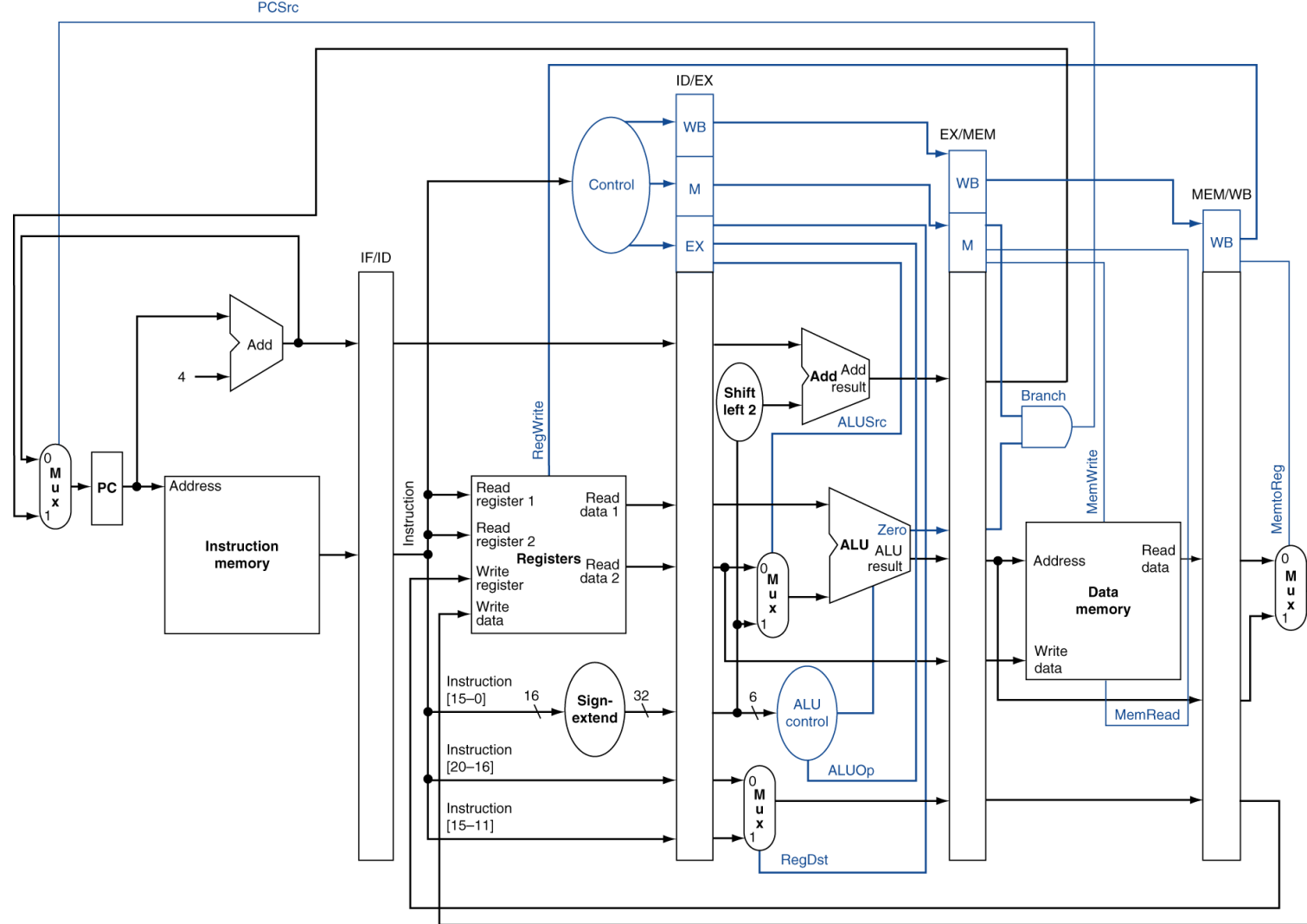


	EX Stage				MEM Stage			WB Stage	
	RegDst	ALUOp1	ALUOp0	ALUSrc	Brch	MemRead	MemWrite	RegWrite	Mem toReg
R	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	X	0	0	1	0	0	1	0	X
beq	X	0	1	0	1	0	0	0	X

# Questions on Pipeline Control?

# Dependencies & Forwarding

	Time (in clock cycles) →								
Value of register \$2:	CC 1	CC 2	CC 3	CC 4	CC 5	CC 6	CC 7	CC 8	CC 9
	10	10	10	10	10/-20	-20	-20	-20	-20

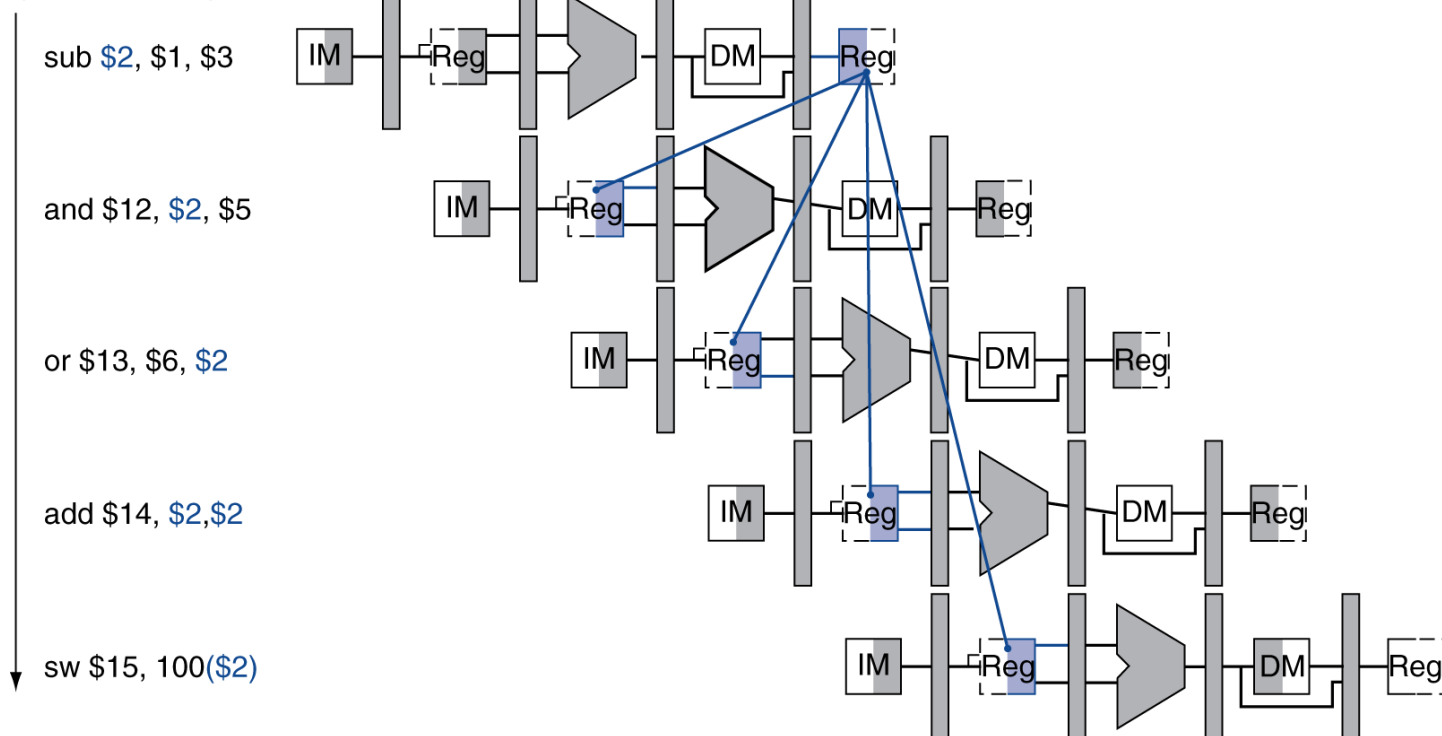Program  
execution  
order  
(in instructions)




# We can best solve **these** data hazards

A. By stalling.

B. By forwarding.

C. By combining forwards and stalls.

D. By doing something else.

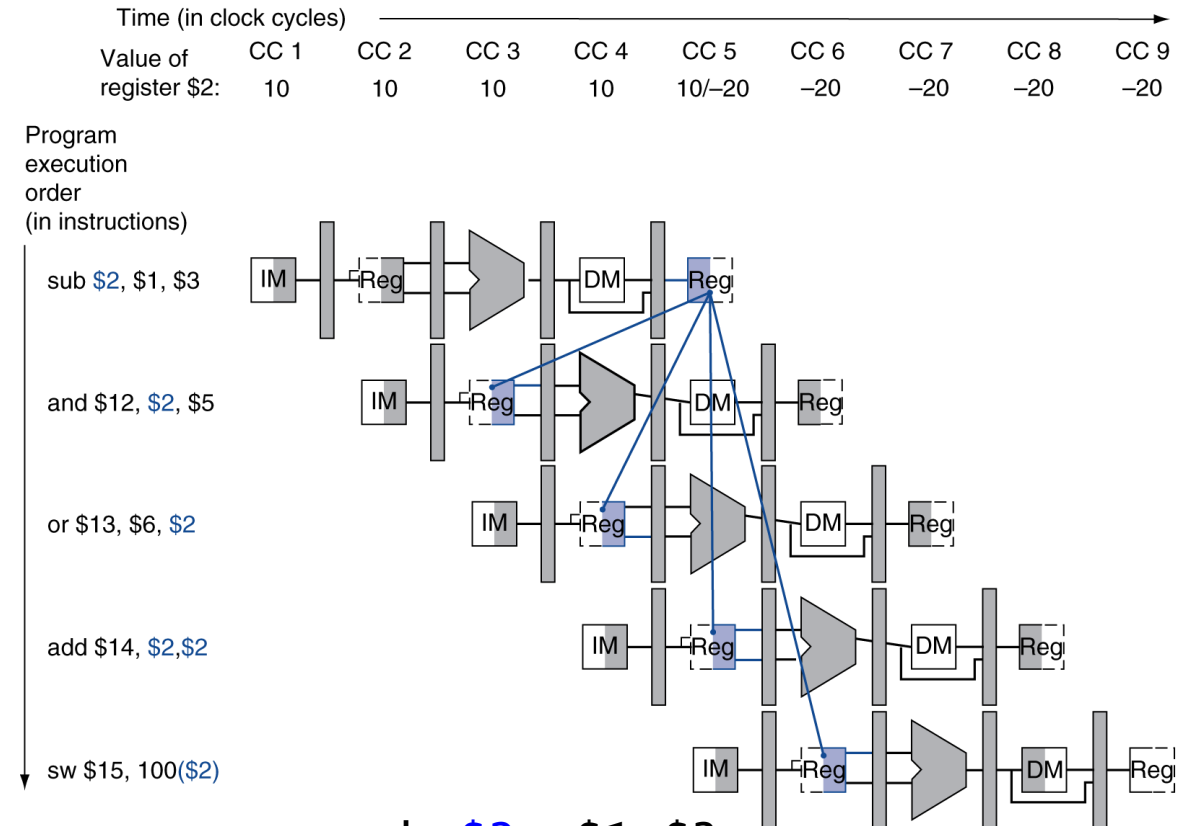

sub \$2, \$1, \$3  
and \$12, \$2, \$5  
or \$13, \$6, \$2  
add \$14, \$2, \$2  
sw \$15, 100(\$2)

# Data Hazards in ALU Instructions

- Consider this sequence:

```
sub  $2, $1, $3  
and  $12, $2, $5  
or   $13, $6, $2  
add  $14, $2, $2  
sw   $15, 100($2)
```

- We can resolve hazards with forwarding
  - How do we detect when to forward?

# Forwarding


## Data path

- Connect the outputs of EX and MEM stages to both ALU inputs controlled by multiplexers

## Control path

- Pass rs, rt, and rd register numbers through the pipeline registers
- Add a forwarding unit to control the multiplexers
  - Depends on RegWrite and rs/rt/rd from various stages

# Detecting the Need to Forward

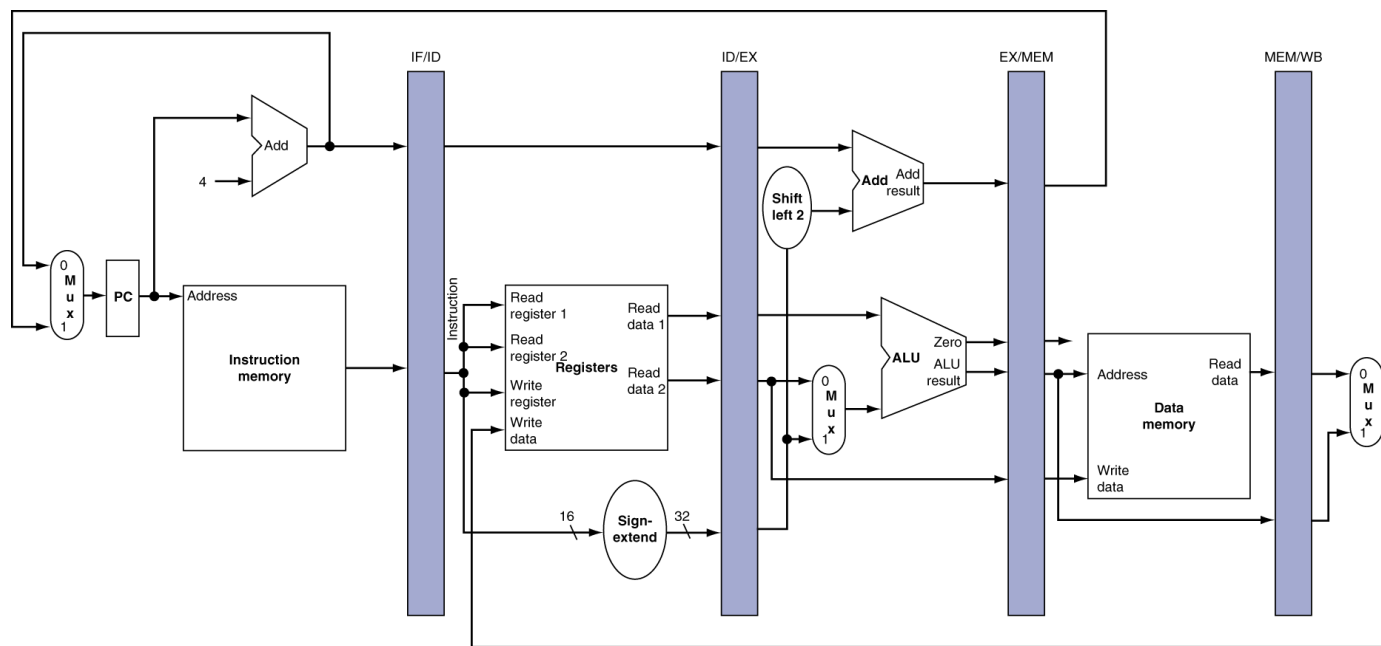

- Data hazards when

1a.  $\text{EX/MEM.RegisterRd} = \text{ID/EX.RegisterRs}$

1b.  $\text{EX/MEM.RegisterRd} = \text{ID/EX.RegisterRt}$

2a.  $\text{MEM/WB.RegisterRd} = \text{ID/EX.RegisterRs}$

2b.  $\text{MEM/WB.RegisterRd} = \text{ID/EX.RegisterRt}$

Fwd from  
EX/MEM  
pipeline reg


Fwd from  
MEM/WB  
pipeline reg

# Detecting the Need to Forward

- But only if forwarding instruction will write to a register!
  - EX/MEM.RegWrite, MEM/WB.RegWrite
- And only if Rd for that instruction is not \$zero
  - EX/MEM.RegisterRd  $\neq$  0,  
MEM/WB.RegisterRd  $\neq$  0




# Forwarding Paths

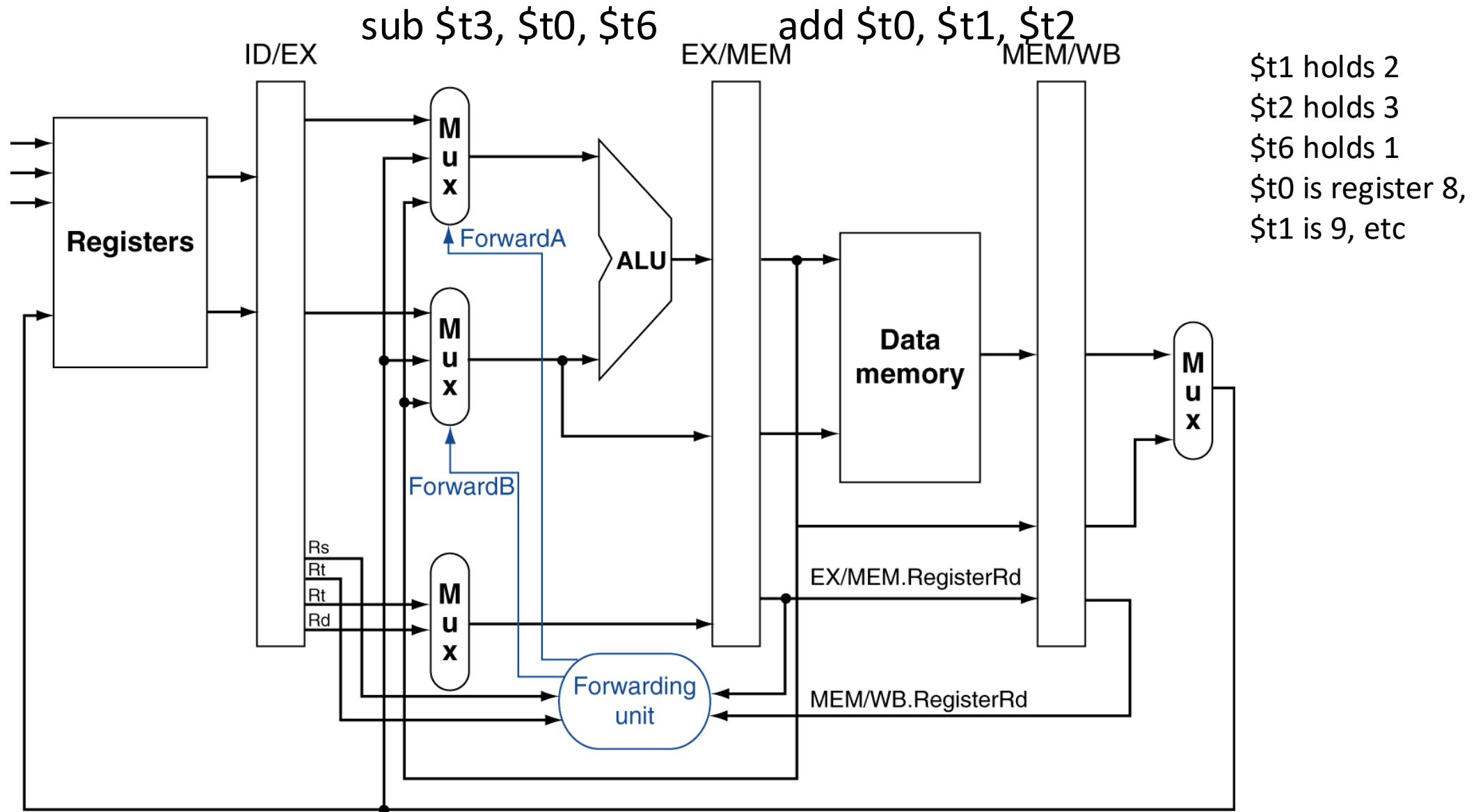

b. With forwarding



# Datapath with Forwarding

 

# Reading

- Next lecture: Pipelined Datapath
  - Section 5.7