



CSCI 210: Computer Architecture

Lecture 25: Data Path 2

Stephen Checkoway


Slides from Cynthia Taylor

CS History: Intel 4004

  


- First commercially available microprocessor (single chip with both data processing logic and control)
- Released in 1971
- Had 12-bit addresses, 8-bit instructions, and 4-bit data words
- 16 4-bit registers
- Designed for Binary-Coded Decimal, in which every decimal digit is stored as a 4-bit value
 - Support for BCD is still present in x86

Datapath (still simplified a bit)

 


addi \$t1, \$t0, -1

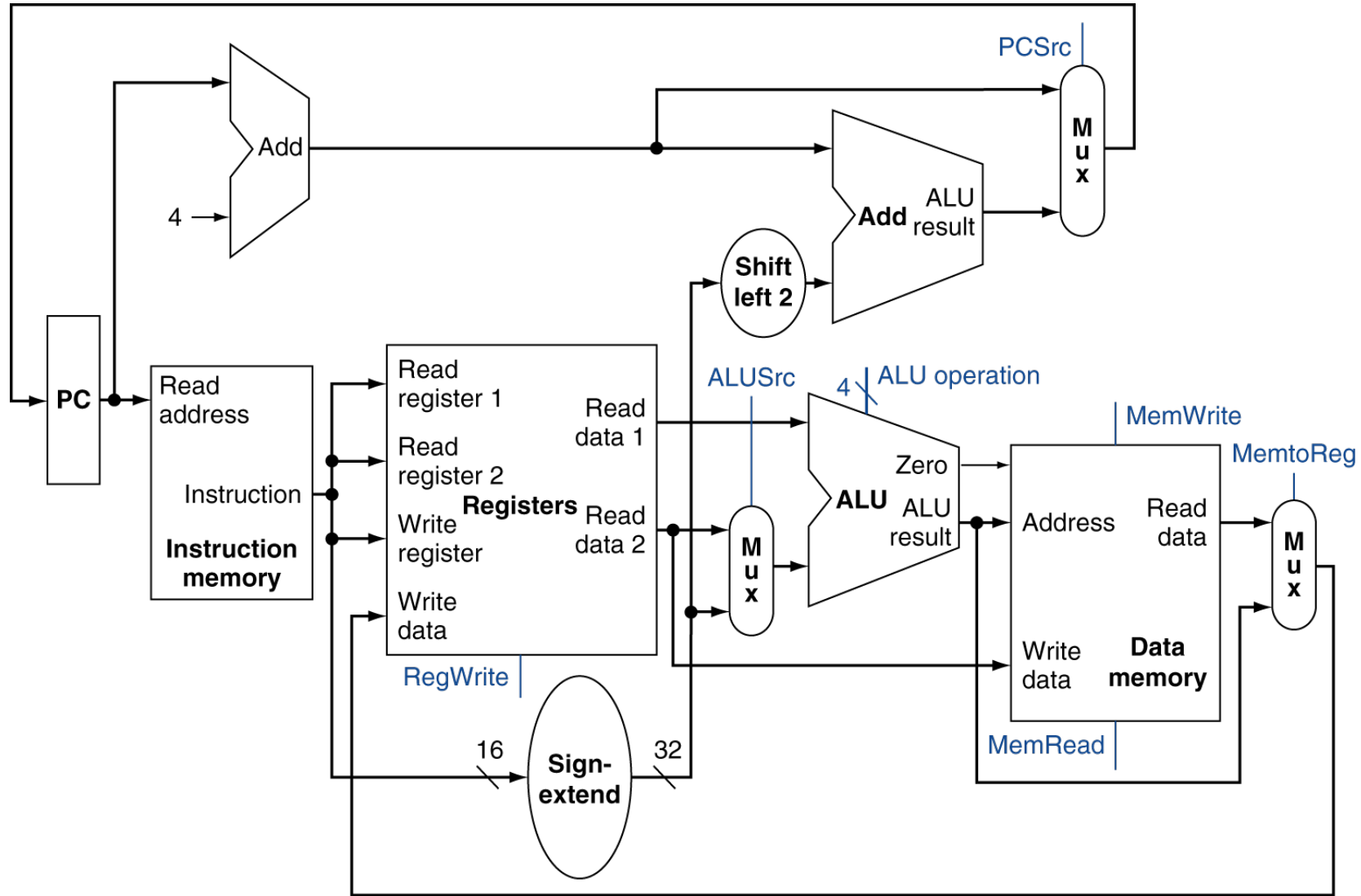

\$t0 holds 10

op = 0x08	rs = 8	rt = 9	imm = 0xFFFF
-----------	--------	--------	--------------

What do we need to add to support ori?

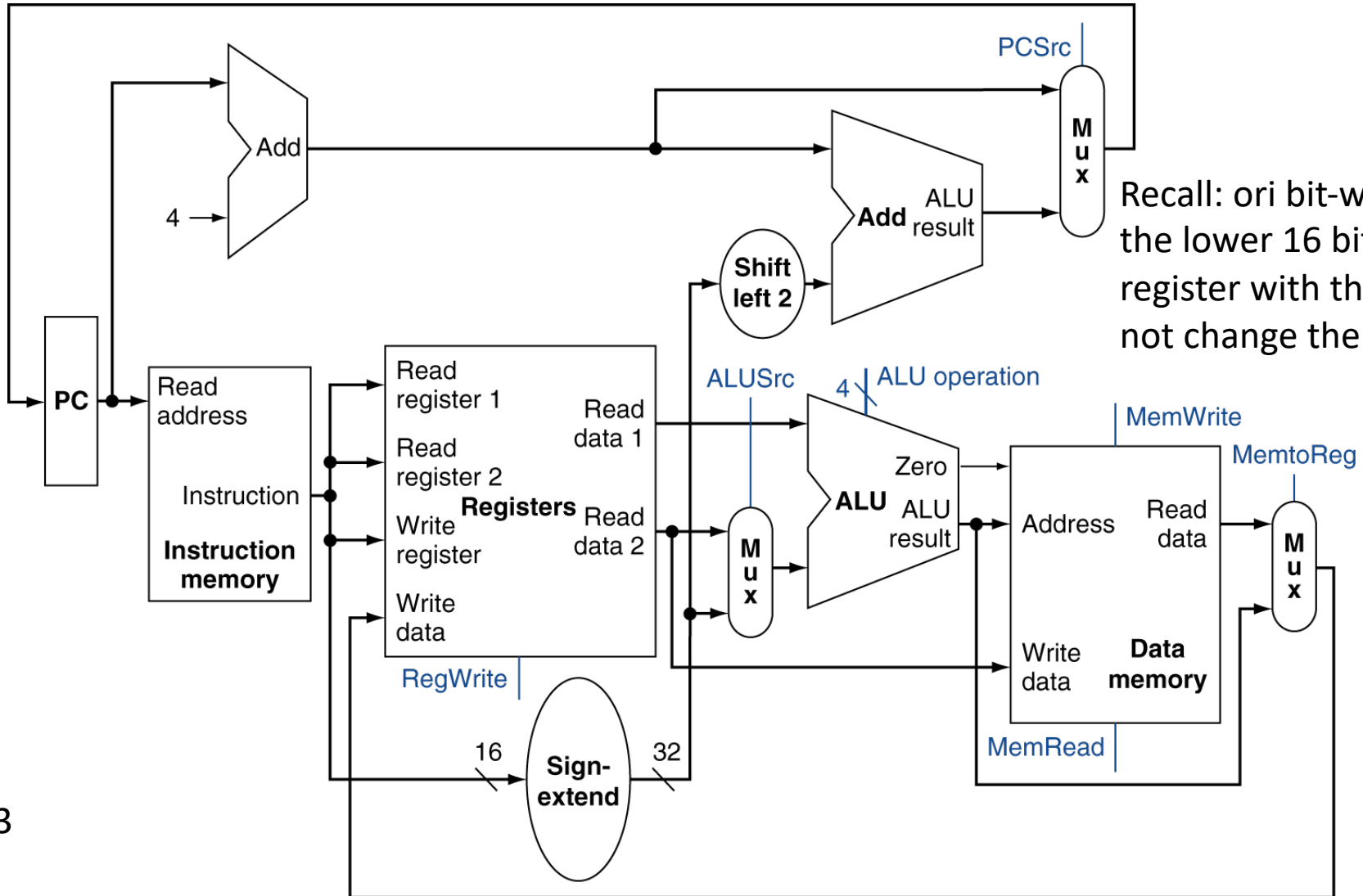


Recall: ori bit-wise ors the lower 16 bits of the specified register with the immediate. It does not change the upper 16 bits.

ori \$t0, \$t1, 0x8003
 \$t1 holds 5


op = 0x0D	rs = 9	rt = 8	imm = 0x8003
-----------	--------	--------	--------------

Imagine a slightly different architecture with an ori instruction that sign-extends its immediate value. If \$t1 has value 5, what value does \$t0 have after `ori $t0, $t1, 0x8003`

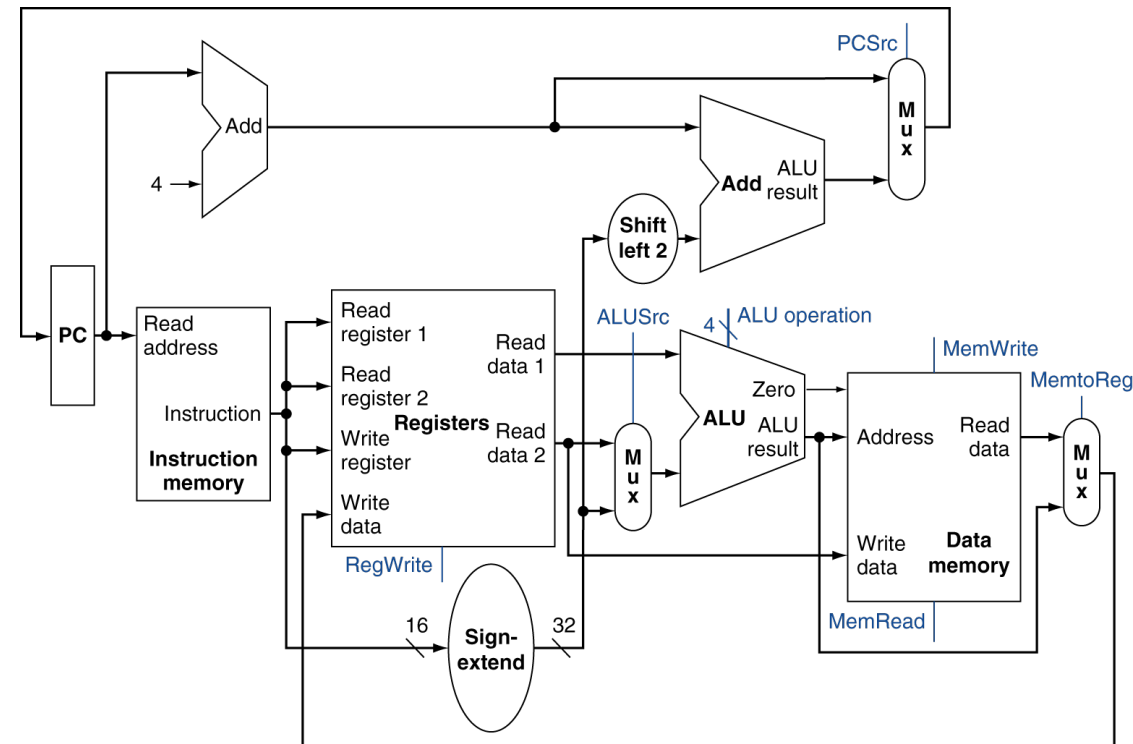- A. 0x00008005
- B. 0x00008007
- C. 0x88888007
- D. 0x80008005
- E. 0xFFFF8007



sw \$t1, 8(\$t0)

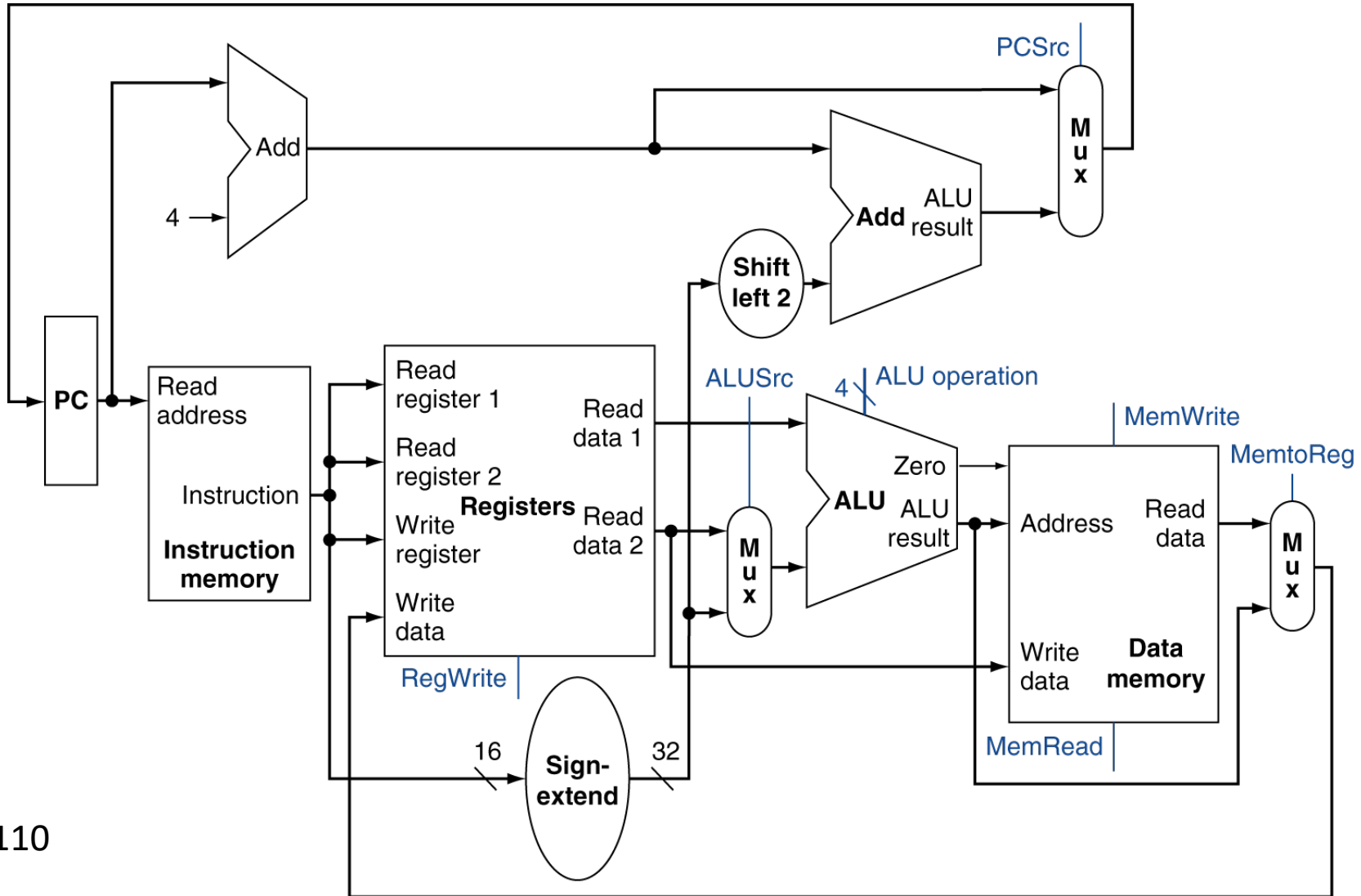


\$t0 holds 0x07AB8110

\$t1 holds 5

op = 0x2B	rs = 8	rt = 9	imm = 0x0008
-----------	--------	--------	--------------

beq \$s0, \$t0, label

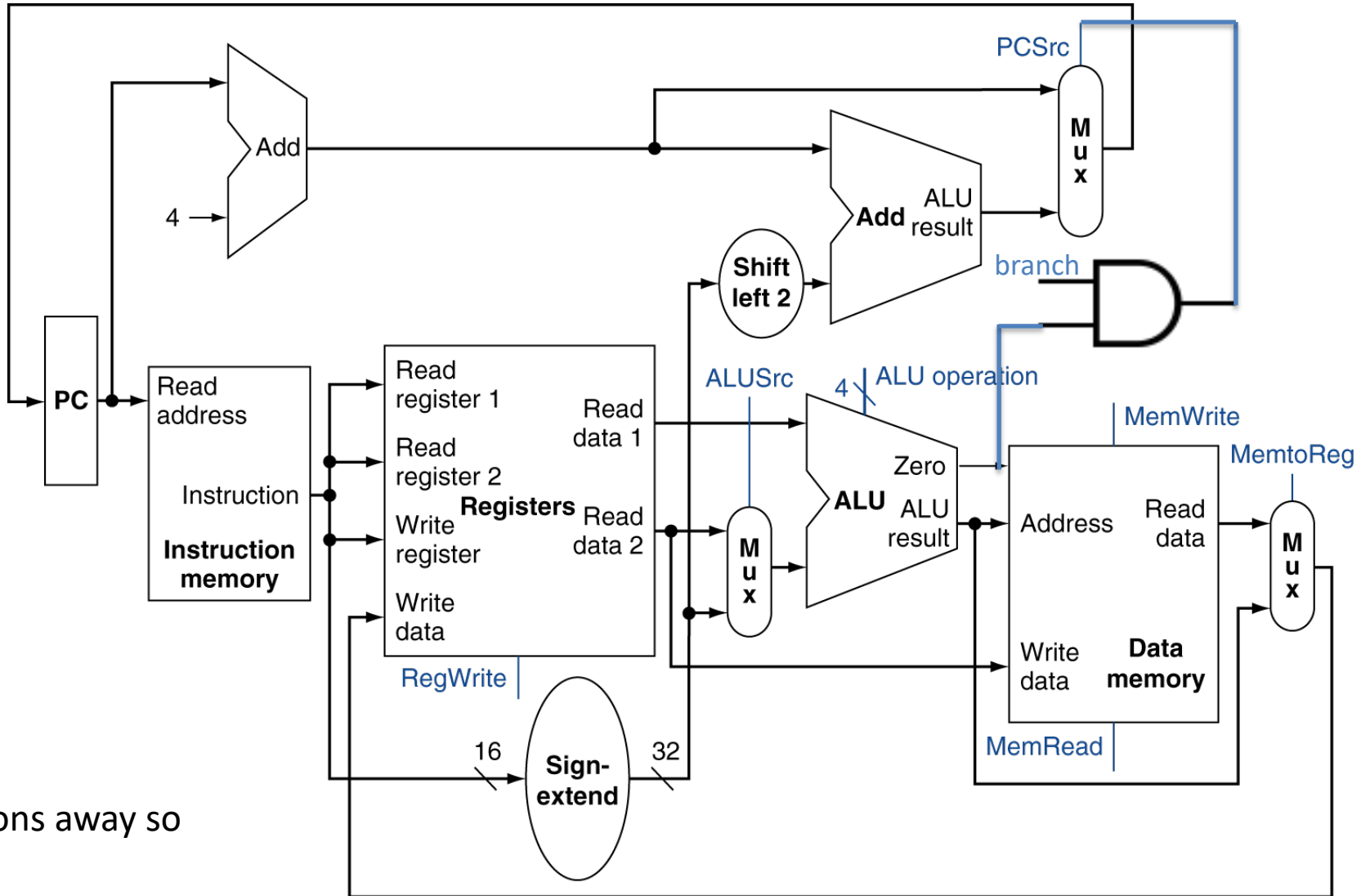

\$s0 holds 10
\$t0 holds 10
label is 33 instructions away so
offset = 0x0020

op = 0x2B	rs = 16	rt = 8	imm = 0x0020
-----------	---------	--------	--------------

Composing the Elements

- Data path executes one instruction in one clock cycle
 - Each data path element can only do one function at a time
 - Hence, we need separate instruction and data memories, ALU and adders, etc
- Use multiplexers where alternative data sources are used for different instructions
 - Each multiplexer will need select inputs to choose which input to use as the output

Key Points

- CPU is just a collection of state and combinational logic
- We just designed a very rich processor, at least in terms of functionality
- $ET = IC * CPI * \text{Cycle Time}$
 - Where cycle time is determined by how much work the processor has to do each clock cycle for one iteration of fetch, decode, execute

Reading

- Next lecture: Control Path
 - Section 5.4